

12/18/2007.

Midterm Exam - 2.



MoonFox.

$$1. (a) I_{C1} = I_{C2} = 10 \text{ mA}$$

$$\Rightarrow I_{B1} = \frac{10}{200} = 0.05 \text{ mA}$$

$$I_B = \frac{10}{50} = 0.04 \text{ mA}$$

offset current = 0.01 mA.

$$(b) I_{C1} = 1 \text{ mA} \Rightarrow \text{由題目給 information}$$


$$\therefore U_{BE11} = 0.7 \text{ V}$$

$$\frac{I_{C11}}{I_{C10}} = \frac{I_S e^{\frac{U_{BE11}}{V_T}}}{I_S e^{\frac{U_{BE10}}{V_T}}} \Rightarrow \frac{10^{-3}}{10^{-5}} = e^{\frac{0.7-x}{V_T}} \Rightarrow 0.055 \ln \left| \frac{10^{-3}}{10^{-5}} \right| = 0.7-x$$

$$\Rightarrow x = 0.585 \text{ (V)}$$

$$0.585 + 10^{-3} \times R_4 = 0.7, R_4 = 11.5 \text{ k}\Omega$$

(c)

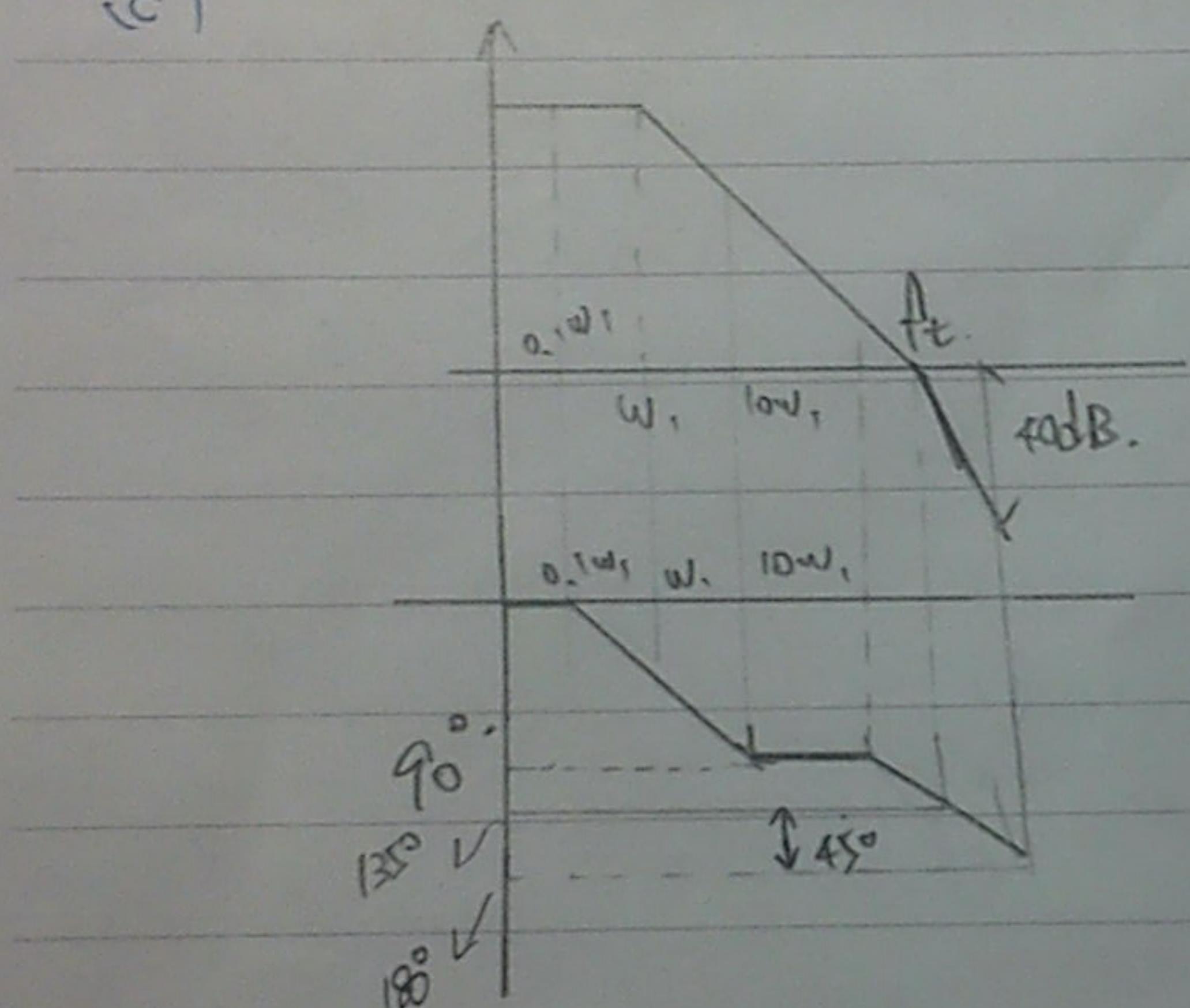 $\Rightarrow f_t$ 為 $\omega_2 = 5 \text{ MHz}$.

$$f_t = \frac{g_m}{2\pi C_o} = f_{-3dB} \times A$$

$$\Rightarrow f_{-3dB} = \frac{5 \text{ MHz}}{10 \text{ dB}} = 28.12 \text{ Hz}$$




$$C_o = \frac{2 \times 10^{-3}}{2\pi \times 5 \times 10^6} = 6.37 \times 10^{-11} \text{ F}$$

2. (a) WTF

$$3. (a) (i) Power = \frac{V_{rms}^2}{R} = \frac{64}{2} \div 100 = 0.32 \text{ (W)}$$

$$(ii) I_L \text{ peak 值} = \frac{V_m}{R} = 0.08 \text{ (A)} \quad \text{又忽略 Q_3 之能}$$
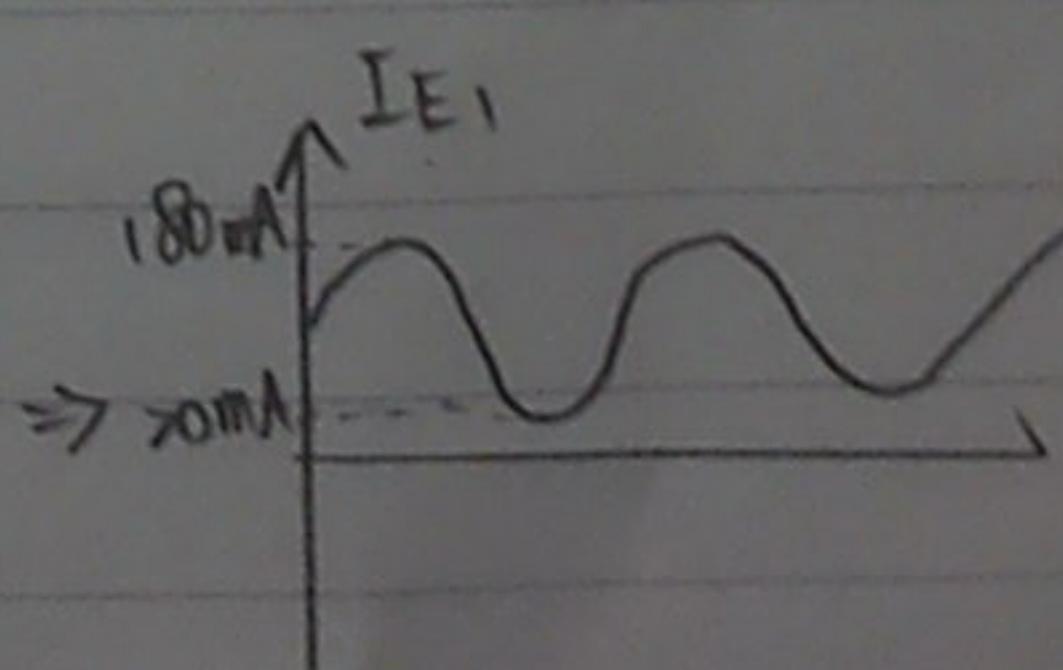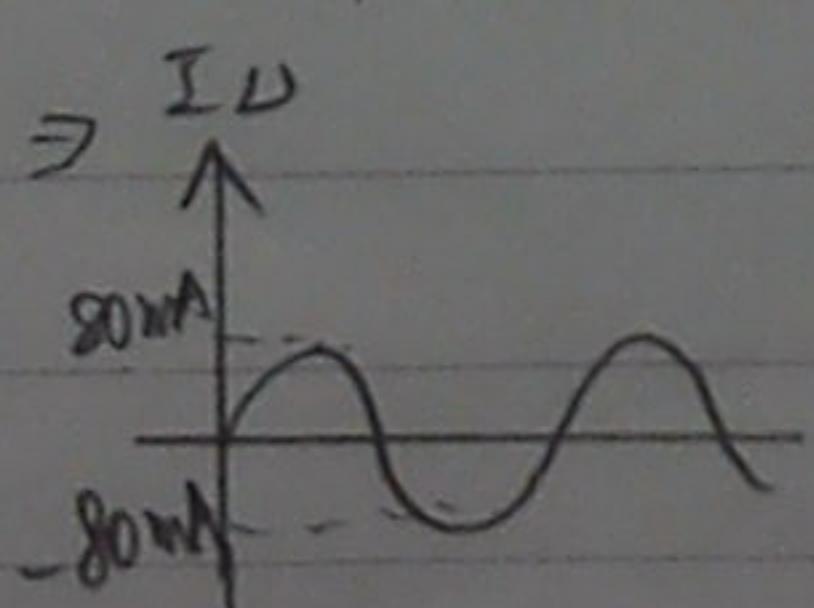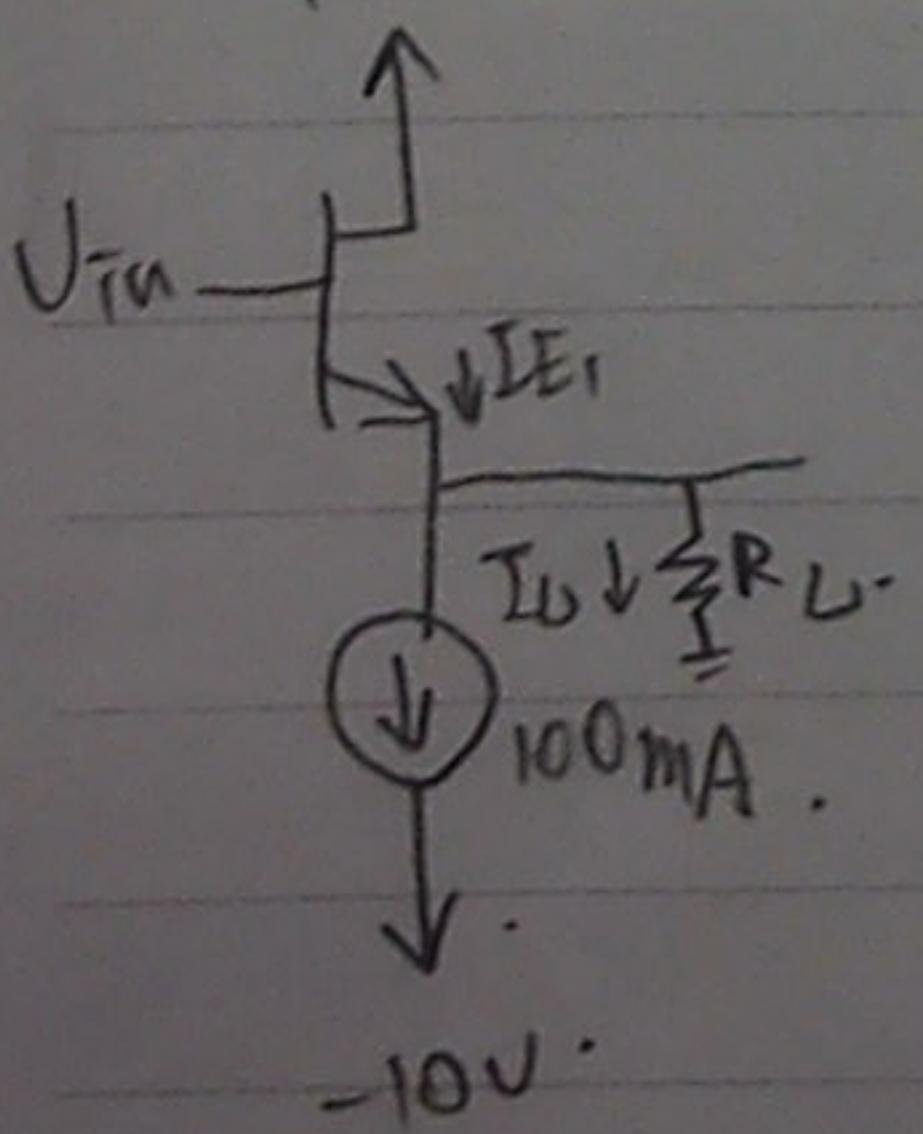
$$\because I_{E1} = I + I_L = 100 \text{ mA} + I_L$$




$$\Rightarrow P_{in} = P_{Q_1} + P_{Q_2}$$

$$= U_{cc} \times I_{Eavg} + (U_{cc}) (-I)$$

$$= 10 \times 100 \text{ m} + 10 \times 100 \text{ m} \quad (\text{國立成功大學論文用紙})$$

$$= 2 \text{ (W)}$$
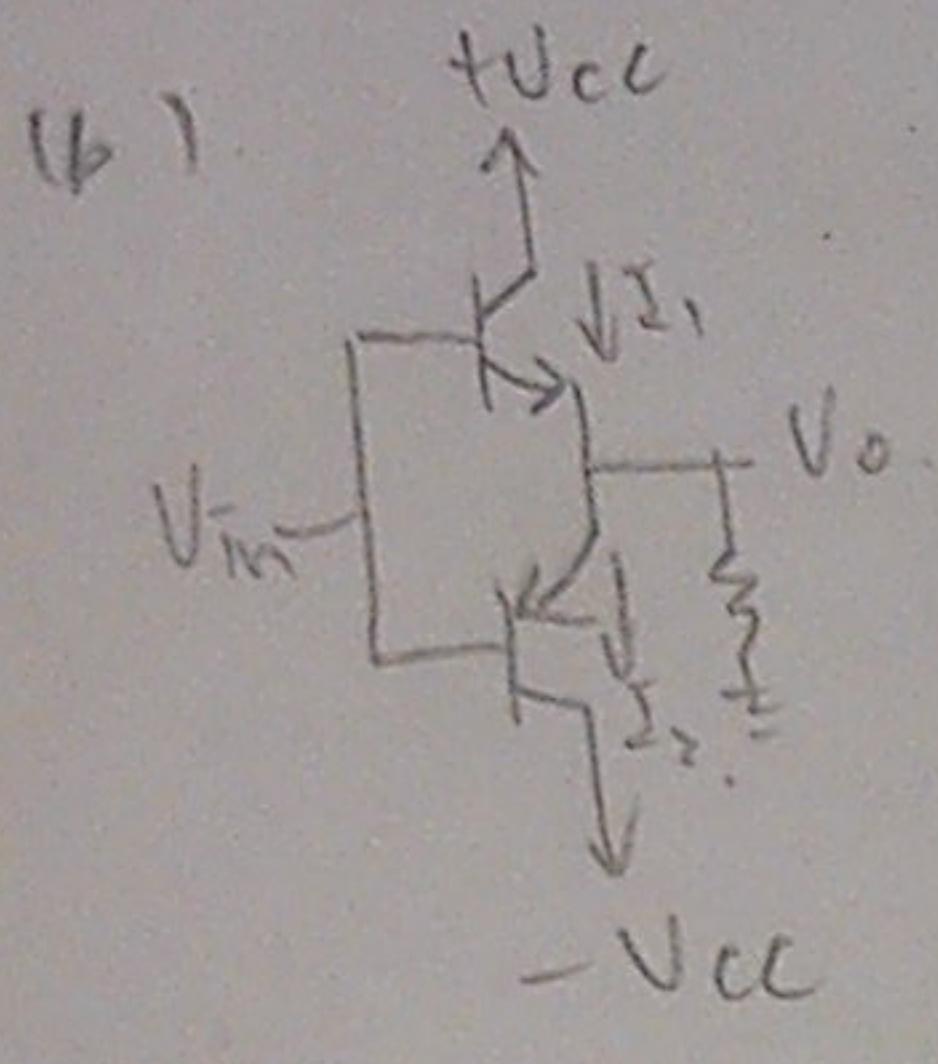
$$\text{iii) efficiency} = \frac{0.32}{2} \times 100\% = 16\%.$$



不考慮 crossover distortion.

$V_o \text{ max 為 } V_{cc}$,

$$V_o \left\{ \begin{array}{l} V_o = V_{cc} \sin(\omega t) \\ I_o = I_o \sin(\omega t) \end{array} \right.$$

$$P_o = I_{rms} \cdot V_{rms} = \frac{V_{cc} I_o}{2}$$

$$P_{in} = I_{avg} \times V_{cc} \times 2 \\ = \frac{\pi}{4} I_o V_{cc}$$

$$\eta_{max} = \frac{P_o}{P_{in}} = \frac{\frac{V_{cc} I_o}{2}}{\frac{\pi}{4} I_o V_{cc}} = 78.5\%$$

4. (a) $P_{max} = \frac{T_{Jmax} - TA}{\theta_{JA}} = \frac{100}{62.5} = 1.6W$

(b) $T_S = TA + P \times \theta_{SA} = 50 + 1.6 \times 4 = 56.4^\circ C$

$$T_C = T_S + P \times \theta_{CS} = 56.4 + 1.6 \times 0.5 = 57.2^\circ C$$


(c) infinite heat sink $\Rightarrow \theta_{CA} = 0$
 $\Rightarrow \theta_{JA} = \theta_{JC}$.

$$\theta_{JC} = 62.5 - 0.5 - 4 = 58^\circ C/W$$

$$P_{max} = \frac{T_{Jmax} - TA}{\theta_{JC}} = \frac{100}{58} = 1.724 (\text{W})$$

12/09/2008 Mid - 2

MoonFox

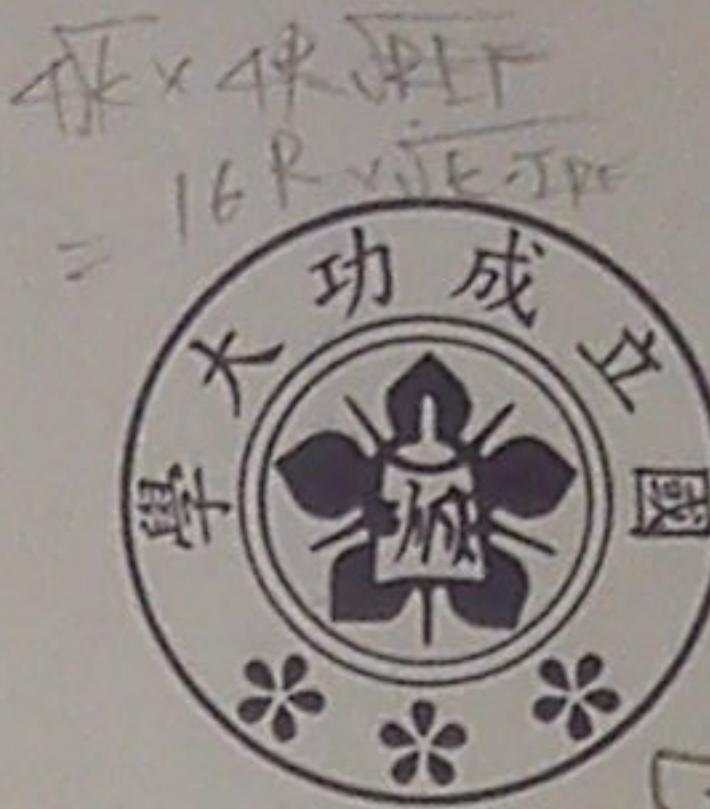

(20%)

$$1. \text{ (a)} I_{REF} = k \times (U_{GSI} - V_t)^2$$

$$\Rightarrow \sqrt{\frac{I_{REF}}{k}} + V_t = U_{GSI}$$

$$I_{out} = 4k \times (U_{GSZ} - V_t)^2$$

$$\Rightarrow \sqrt{\frac{I_{out}}{4k}} + V_t = U_{GSZ}$$

$$\Rightarrow U_{GSI} = U_{GSZ} + I_{out} \times R$$

$$\sqrt{\frac{I_{REF}}{k}} = \sqrt{\frac{I_{out}}{4k}} + I_{out} \times R \quad \text{令 } \sqrt{I_{out}} = x$$

$$x = \frac{-\frac{1}{4k} + \sqrt{\frac{1}{16k^2} + 4R\frac{I_{REF}}{k}}}{2R} = \frac{-1 + \sqrt{1 + 16R\frac{I_{REF}}{k}}}{4R\sqrt{k}}$$

电流不為負
(取正)

$$I_{out} = \frac{1 - \sqrt{1 + 16R\frac{I_{REF}}{k}} + 1 + 16R\frac{I_{REF}}{k}}{16R^2 k}$$

$$= \frac{1 - \sqrt{1 + 16R\frac{I_{REF}}{k}} + 8R\sqrt{k} \cdot I_{REF}}{8R^2 k}$$

$$(b) \frac{I_{C10}}{I_{REF}} = \frac{I_s \cdot e^{\frac{V_{BE10}}{V_T}}}{I_s \cdot e^{\frac{V_{BE11}}{V_T}}} = e^{\frac{V_{BE10} - V_{BE11}}{V_T}}$$

$$\times V_{BE11} - V_{BE10} = I_{C10} \times 5k$$

$$\Rightarrow I_{C10} = I_{REF} \times e^{\frac{-\sum C_{10} \times 5k}{V_T}} = 10^{-3} \times e^{-I_C \times 2 \times 10^5}$$

$$\ln(I_C \times 10^3) = -I_C \times 2 \times 10^5$$

$$I_C = \frac{-\ln(I_C \times 10^3)}{2 \times 10^5}$$

$$\text{迭代法, 設 } I_C = 10^{-5} A, I_C = \frac{-\ln(10^{-5} \times 10^3)}{2 \times 10^5} = 2.3 \times 10^{-5}$$

$$\text{設 } I_C = 2.3 \times 10^{-5} A, I_C = 1.886 \times 10^{-5}$$

$$\text{設 } I_C = 1.886 \times 10^{-5}, I_C = 1.985 \times 10^{-5}$$

$$\text{設 } I_C = 1.985 \times 10^{-5}, I_C = 1.96 \times 10^{-5}$$

$$I_C = 1.96 \times 10^{-5}, I_C = 1.966 \times 10^{-5}$$

$$I_C = 1.966 \times 10^{-5}, I_C = 1.965 \times 10^{-5}$$



⋮

$$\Rightarrow I_{C10} = 1.965 \times 10^{-5} (A)$$

2. 3. WTF.

A. (P).

小試題：

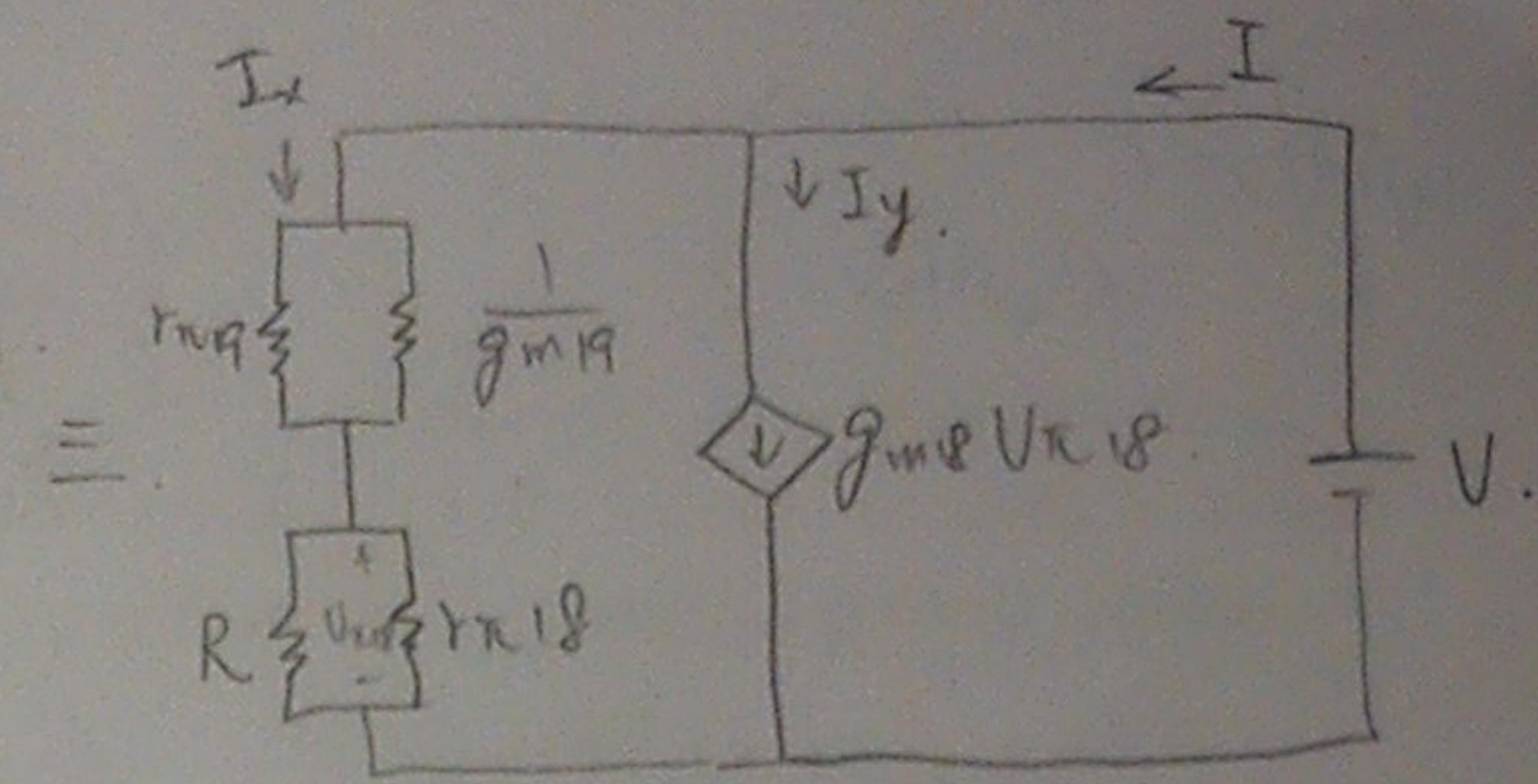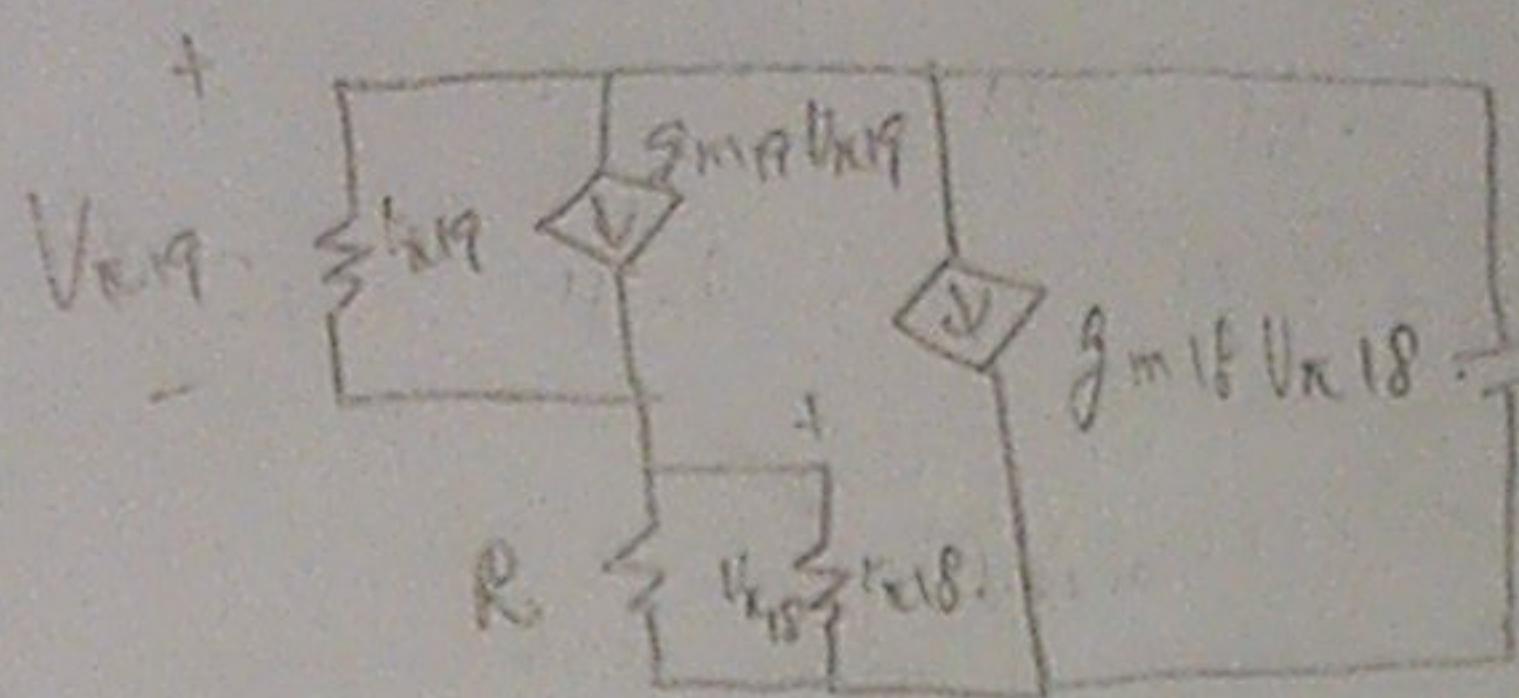

$$\Rightarrow V = V_{X19} + V_{X18}.$$

$$V_{X18} = I_x \cdot (R // r_{m18}).$$

$$I_y = g_{m18} \cdot (R // r_{m18}) \cdot I_x$$



$$V = I_x \cdot \left[r_{X19} // \frac{1}{g_{m19}} + (R // r_{m18}) \right] \quad r_{X19} = 312.5 \text{ k}\Omega.$$

$$Z = \frac{V}{I} = \frac{I_x \cdot \left[(r_{X19} // \frac{1}{g_{m19}}) + (R // r_{m18}) \right]}{I_x + g_{m18} \cdot (R // r_{m18}) \cdot I_x}$$

$$= \frac{(r_{X19} // \frac{1}{g_{m19}}) + (R // r_{m18})}{1 + g_{m18} (R // r_{m18})}$$

$$= \frac{7.77 + 17.24 \times 10^3}{1 + 113.78} = 150.26 \text{ }\Omega.$$

(b)

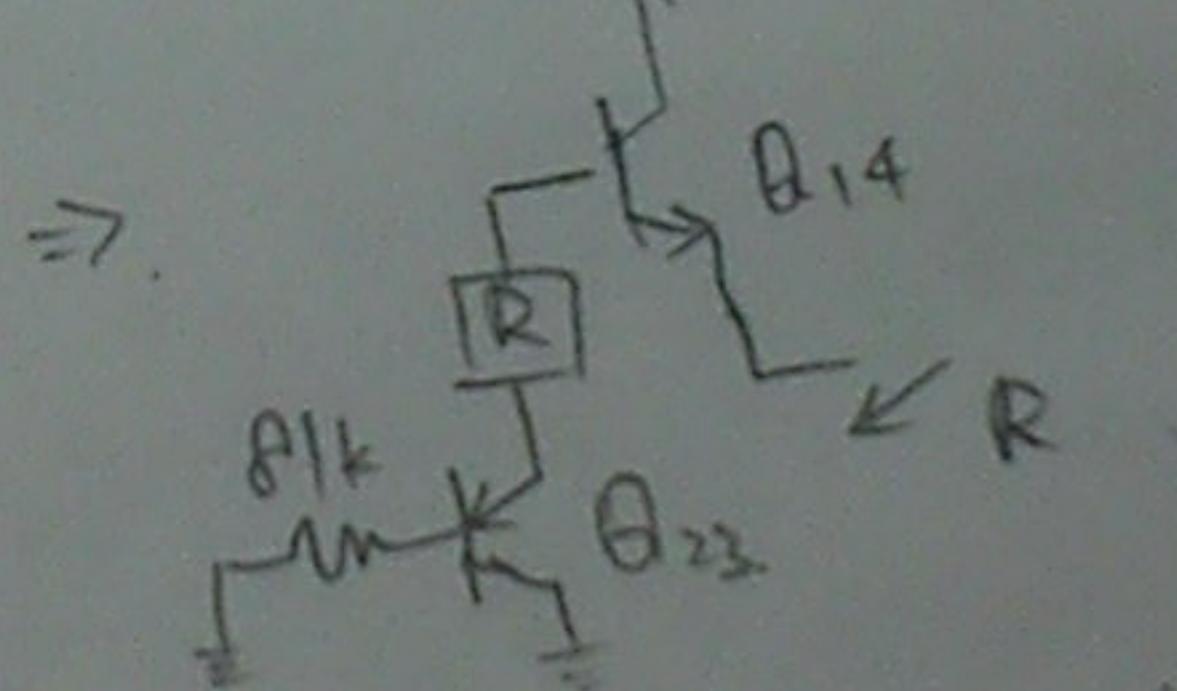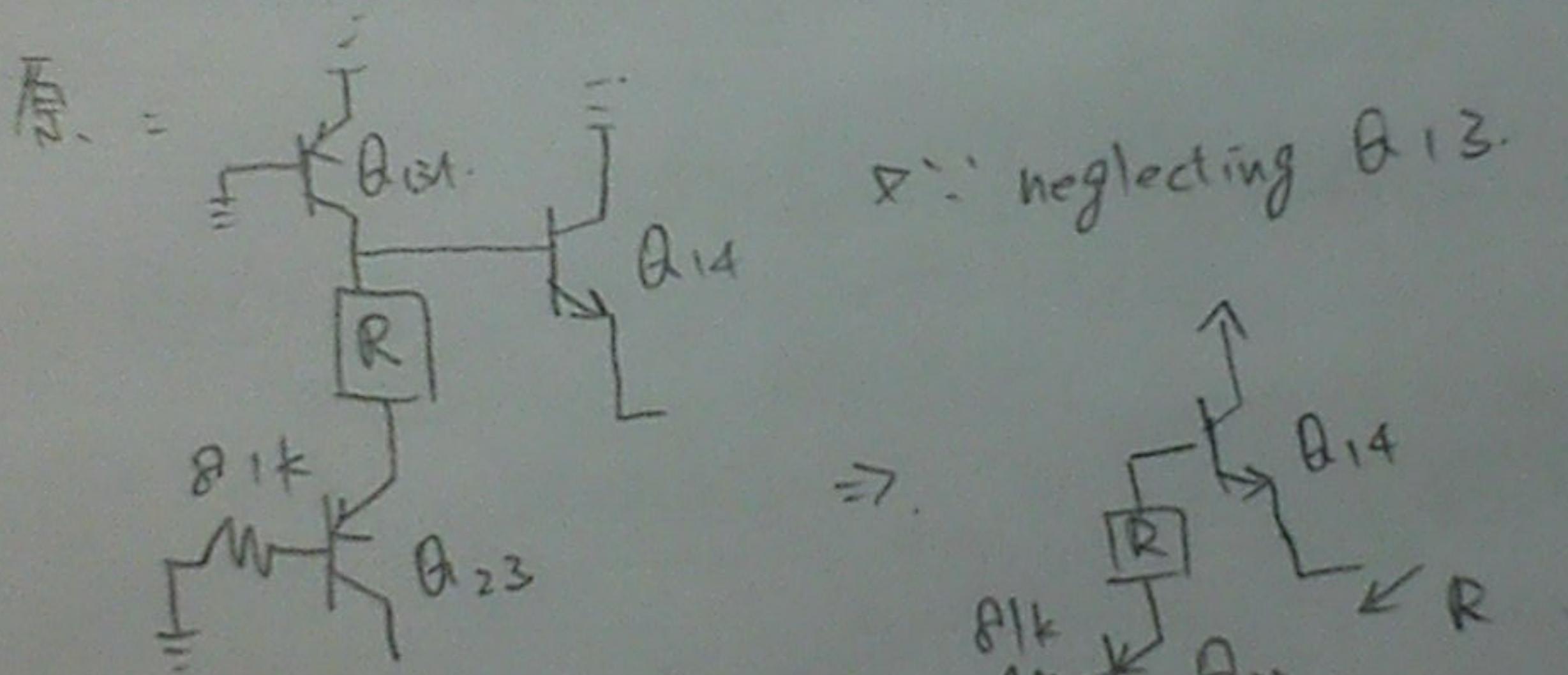

$$R_{out} = \frac{r_{\pi14} + R}{1 + \beta_{14}} + \frac{r_{\pi23} + 81\text{k}}{1 + \beta_{23}}$$

$$= \frac{5000 + 150.26 + \frac{6900 + 81000}{51}}{201}$$

$$= 34.2 \text{ }\Omega.$$

$$r_{\pi14} = \frac{V_T}{I_0} \times \beta = 5 \text{ k}\Omega.$$

$$\beta_{23} = 50.$$

$$r_{\pi23} = \frac{V_T}{I_{023}} \times \beta$$

$$= \frac{0.025}{181 \text{ mA}} \times 50 = 6.9 \text{ k}\Omega$$

S. 6. WTF!

Final - 01/13/2009.

1. 2. 3. WTF!

4. (a) if input = $\bar{I}_1 = I_0 \cos(\omega t)$

$$\text{output } \bar{I}_0 = I_0 + I_1 \cos(\omega t) + I_2 \cos(2\omega t) + I_3 \cos(3\omega t) \dots$$

$$N\text{th harmonic distortion } D_N = \left| \frac{I_N}{I_0} \right|, N = 2, 3, 4 \dots$$

$$\text{total harmonic distortion} = \sqrt{D_2^2 + D_3^2 + D_4^2 \dots}$$

(b) if input = $\bar{I}_1 = I_0 [\cos(\omega_1 t) + \cos(\omega_2 t)]$

$$\text{output } \bar{I}_0 = G \bar{I}_0$$

$$= G I_0 [\cos^2(\omega_1 t) + \cos(\omega_1 t) \cos(\omega_2 t) + \cos^2(\omega_2 t)]$$



$$= G I_0 \left[\frac{1}{2} + \frac{1}{2} \cos(2\omega_1 t) + \frac{1}{2} \cos[(\omega_1 + \omega_2)t] + \frac{1}{2} \cos[(\omega_1 - \omega_2)t] + \frac{1}{2} + \frac{1}{2} \cos(2\omega_2 t) \right]$$

\Rightarrow 頻率有 $\omega_1, \omega_2, 2\omega_1, 2\omega_2, \omega_1 + \omega_2, \omega_1 - \omega_2$



↓ inter-modulation distortion.

(c)



class A.

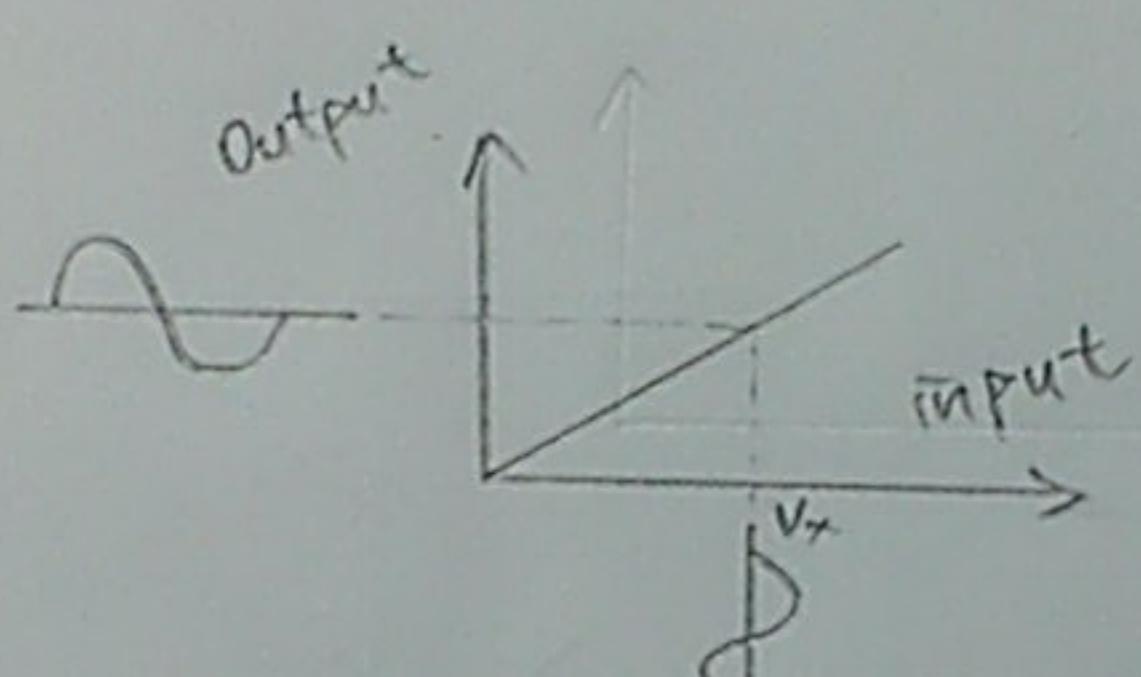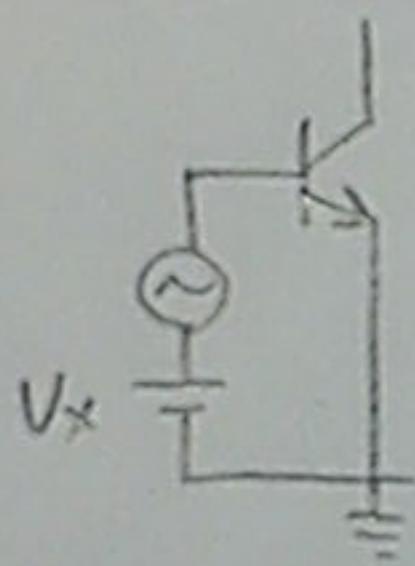

class B

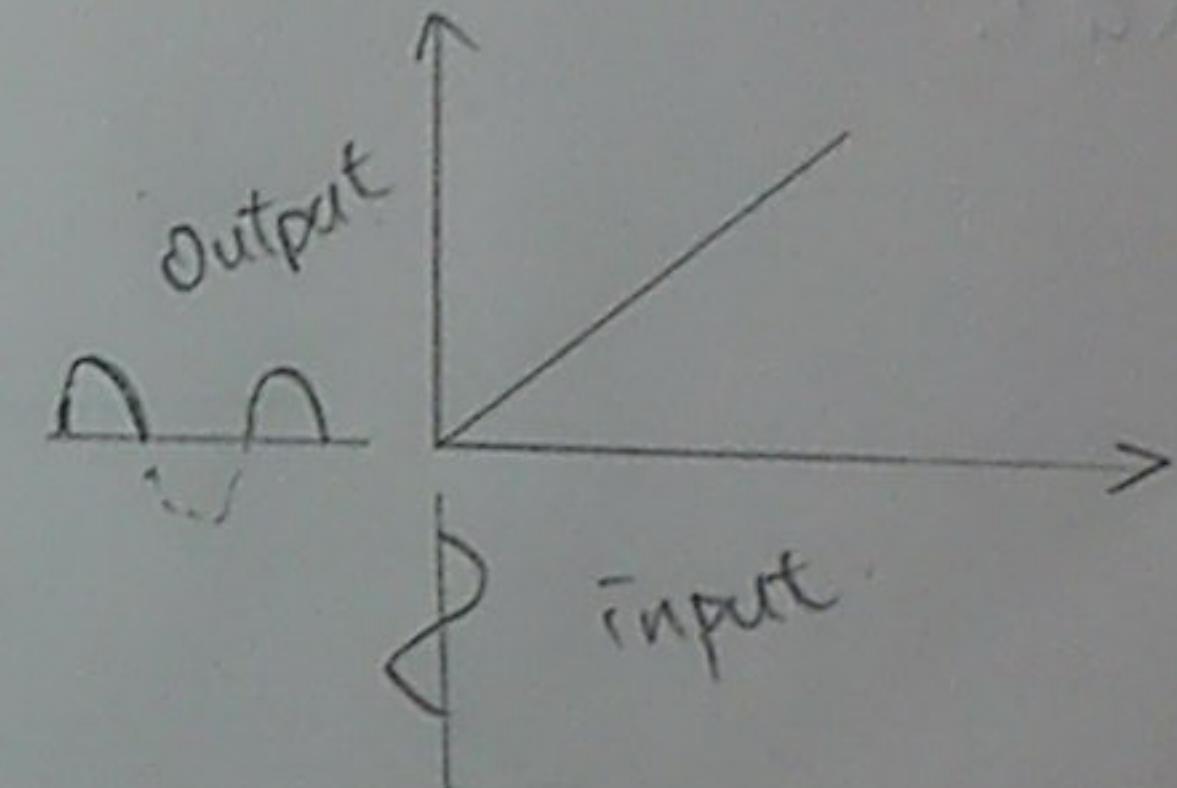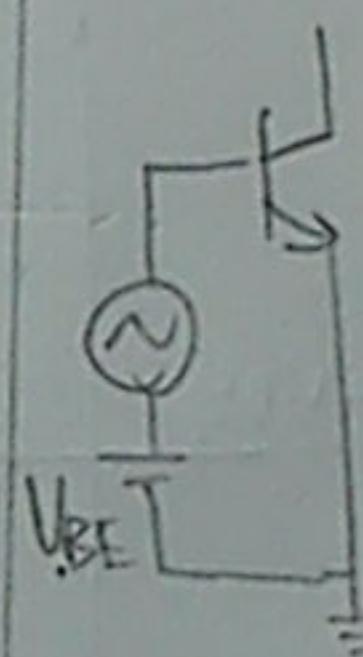


class AB.

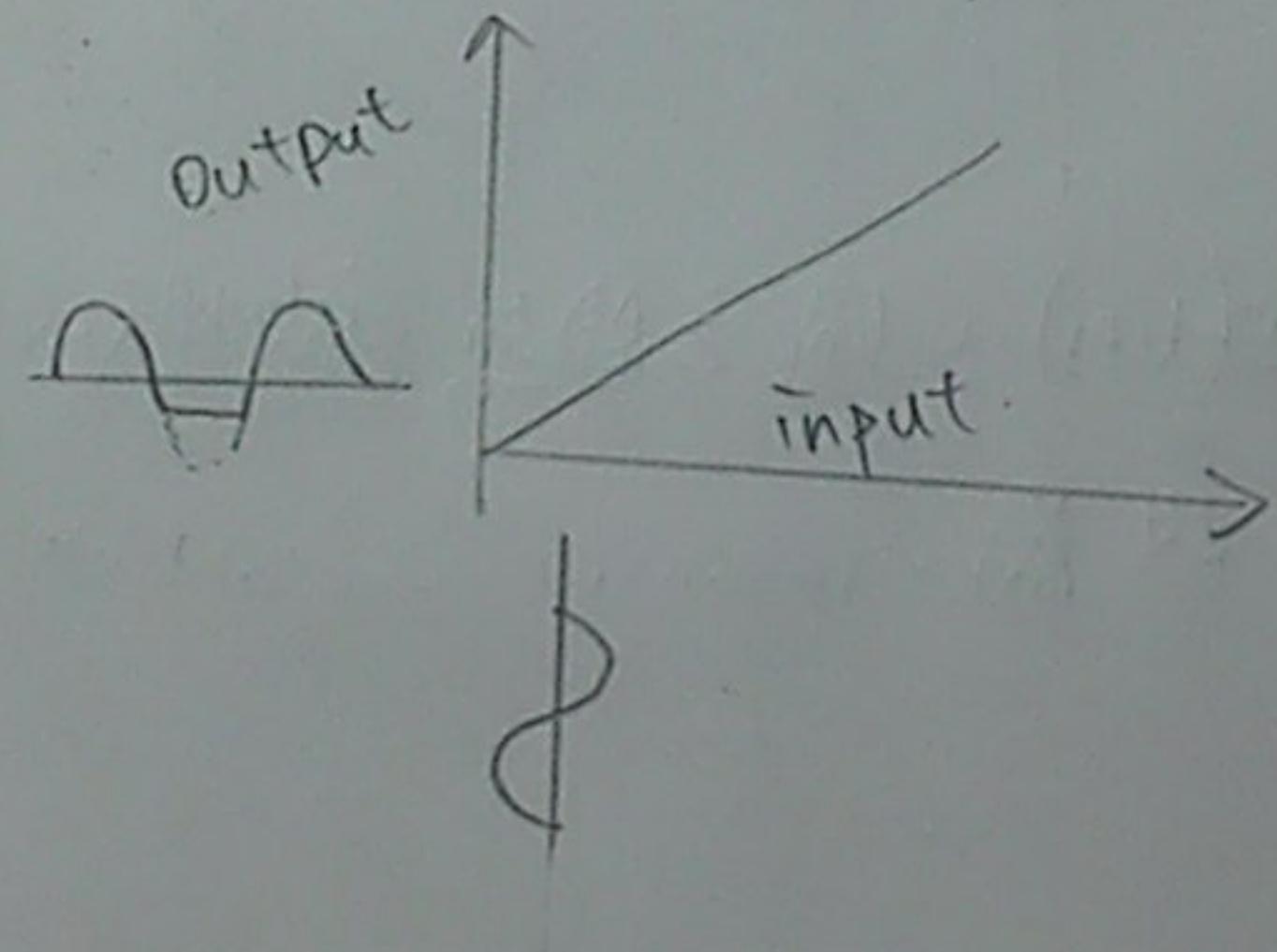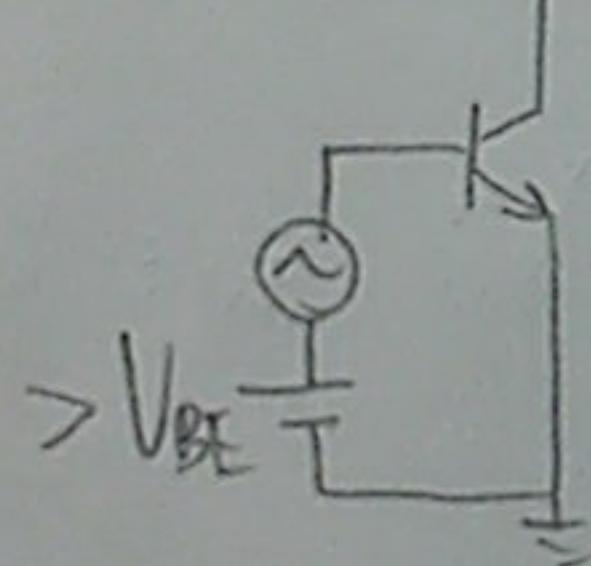

(d).

push-pull

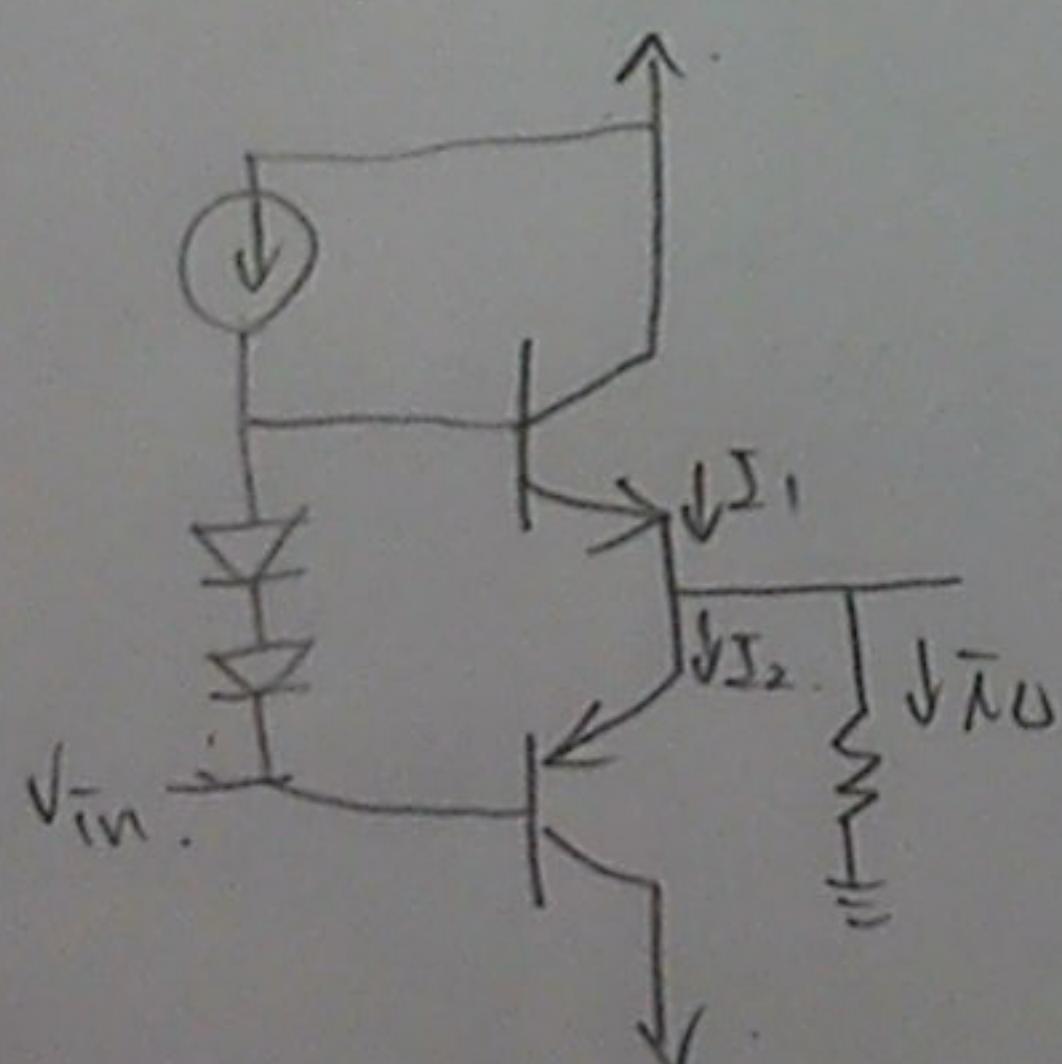


If $\bar{I}_1 = I_0 + I_1 \cos(\omega t) + I_2 \cos(2\omega t) + I_3 \cos(3\omega t) \dots$

$$\because \bar{I}_1(\omega t) = \bar{I}_2(\omega t + \pi)$$

$$\therefore \bar{I}_2 = I_0 - I_1 \cos(\omega t) + I_2 \cos(2\omega t) - I_3 \cos(3\omega t)$$

$$\bar{I}_0 = I_1 - \bar{I}_2 = 2 I_1 \cos(\omega t) + 2 I_3 \cos(3\omega t)$$

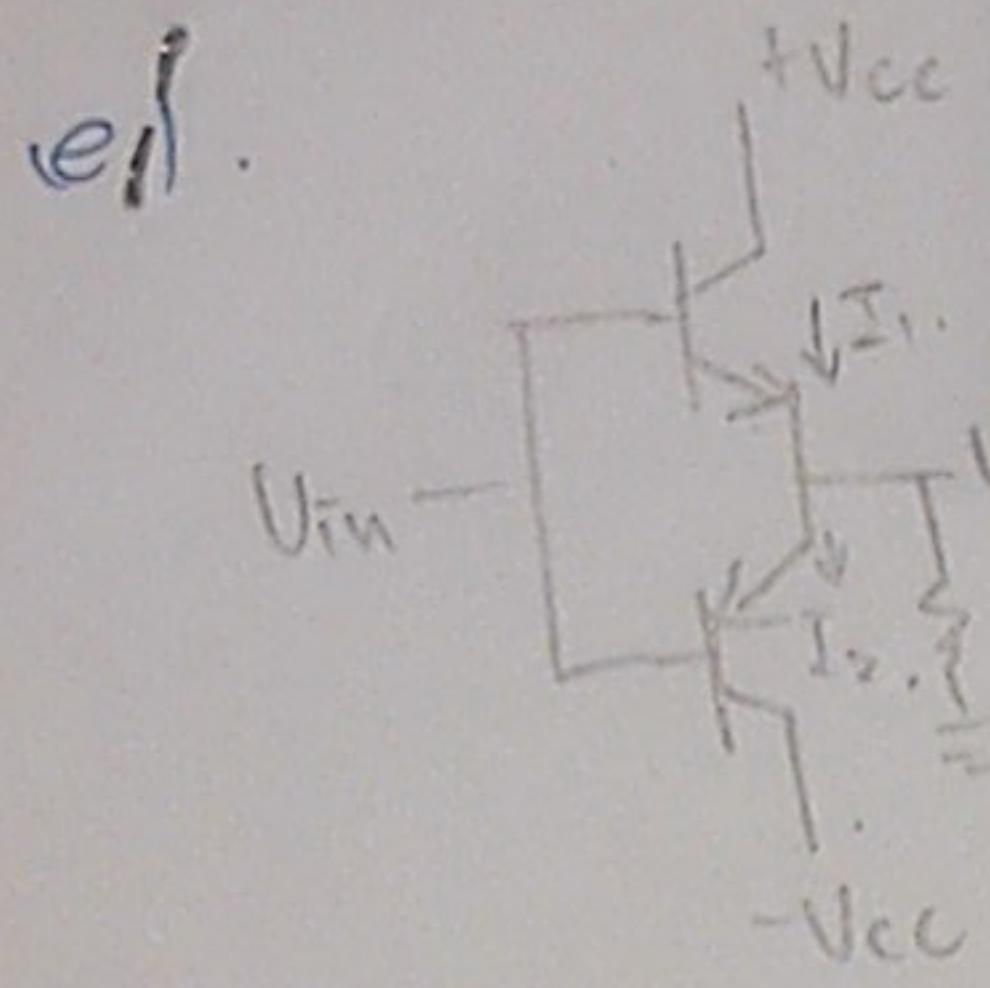
\Rightarrow even-order harmonics are eliminated.



不考慮 crossover distortion

Output: $V_o \leq \text{max 為 } \pm V_{cc}$. $\left\{ \begin{array}{l} V_o = V_{cc} \sin(\omega t) \\ I_o = I_o \sin(\omega t) \end{array} \right.$
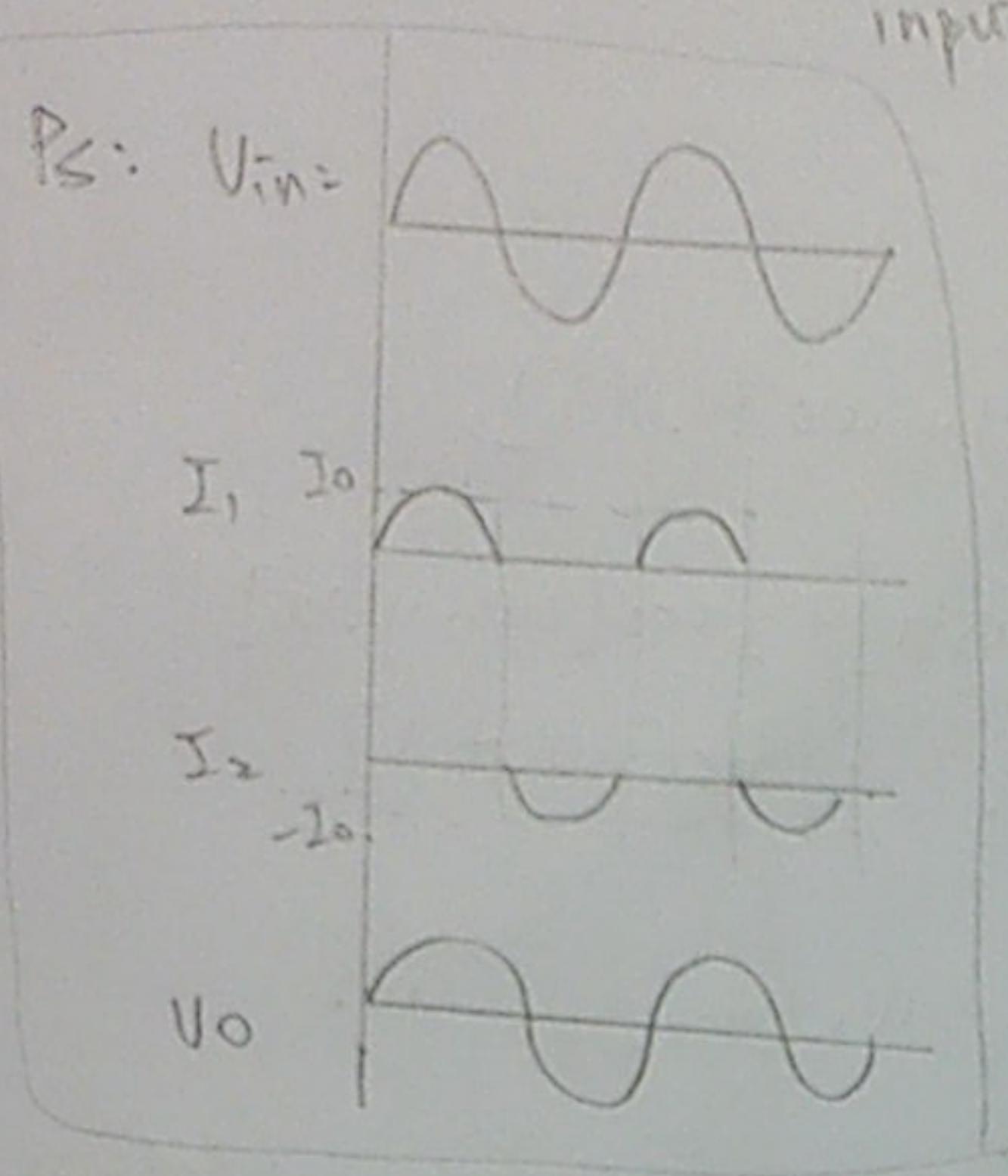
$$P_o = I_{rms} \cdot V_{rms} = \frac{V_{cc}}{\sqrt{2}} \cdot \frac{I_o}{\sqrt{2}} = \frac{V_{cc} I_o}{2}$$



Input: $P_m = I_{avg} \times V_{cc} \times 2$ (因爲上下兩只管子)


($\because V_{cc}$ 為定值, $P=IV$, 故不用 rms 而用 I_{avg})

(最後 $\times 2$ 是因為上下2個BJT)


$$= \left(\frac{1}{\pi} I_o \right) \times V_{cc} \times 2 = \frac{2}{\pi} I_o V_{cc}$$

$$\eta_{max} = \frac{P_{out}}{P_{in}} = \frac{\frac{V_{cc} I_o}{2}}{\frac{2}{\pi} I_o V_{cc}} = \frac{\pi}{4} = 78.5\%$$

5. 例1.

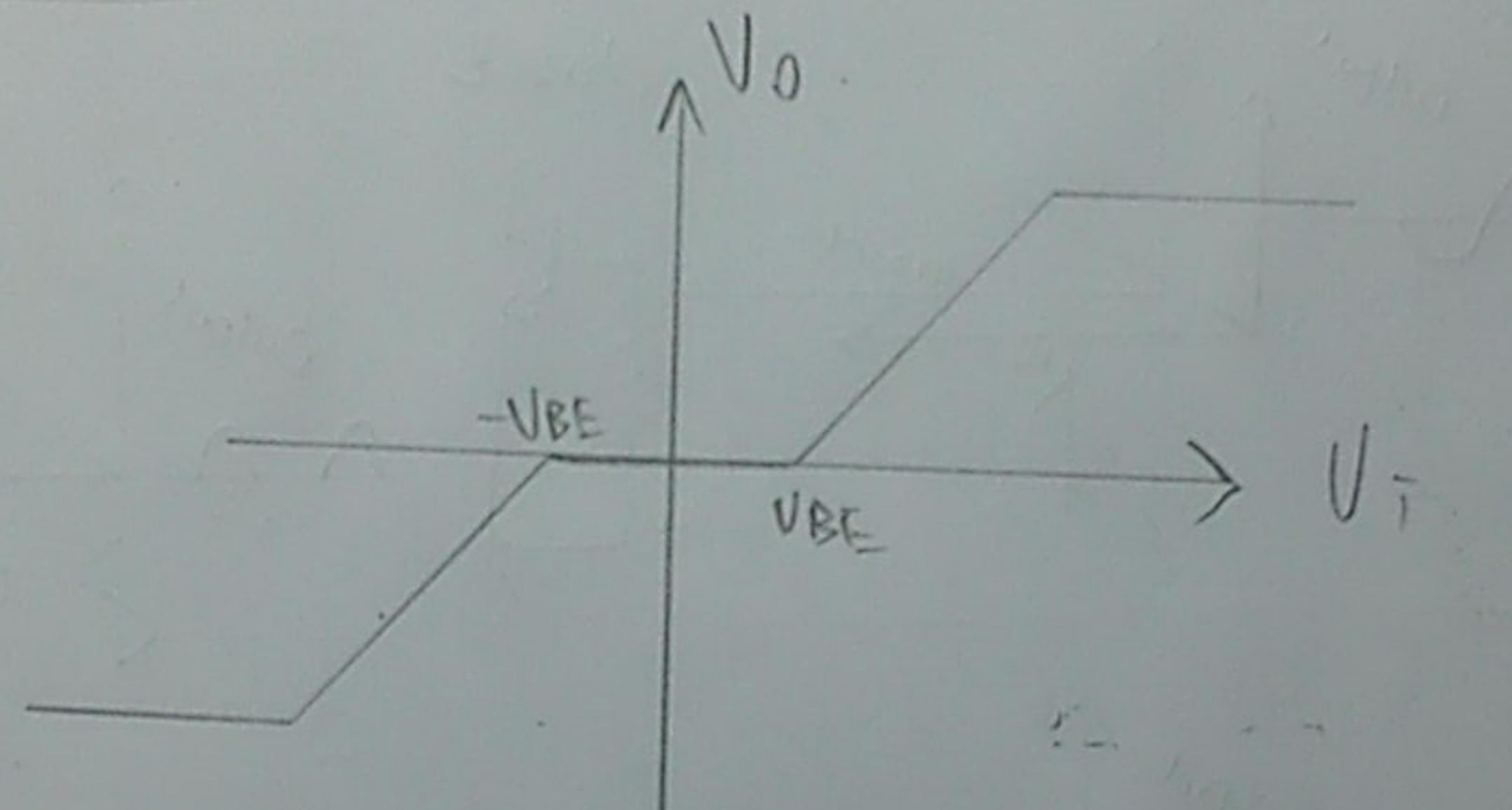

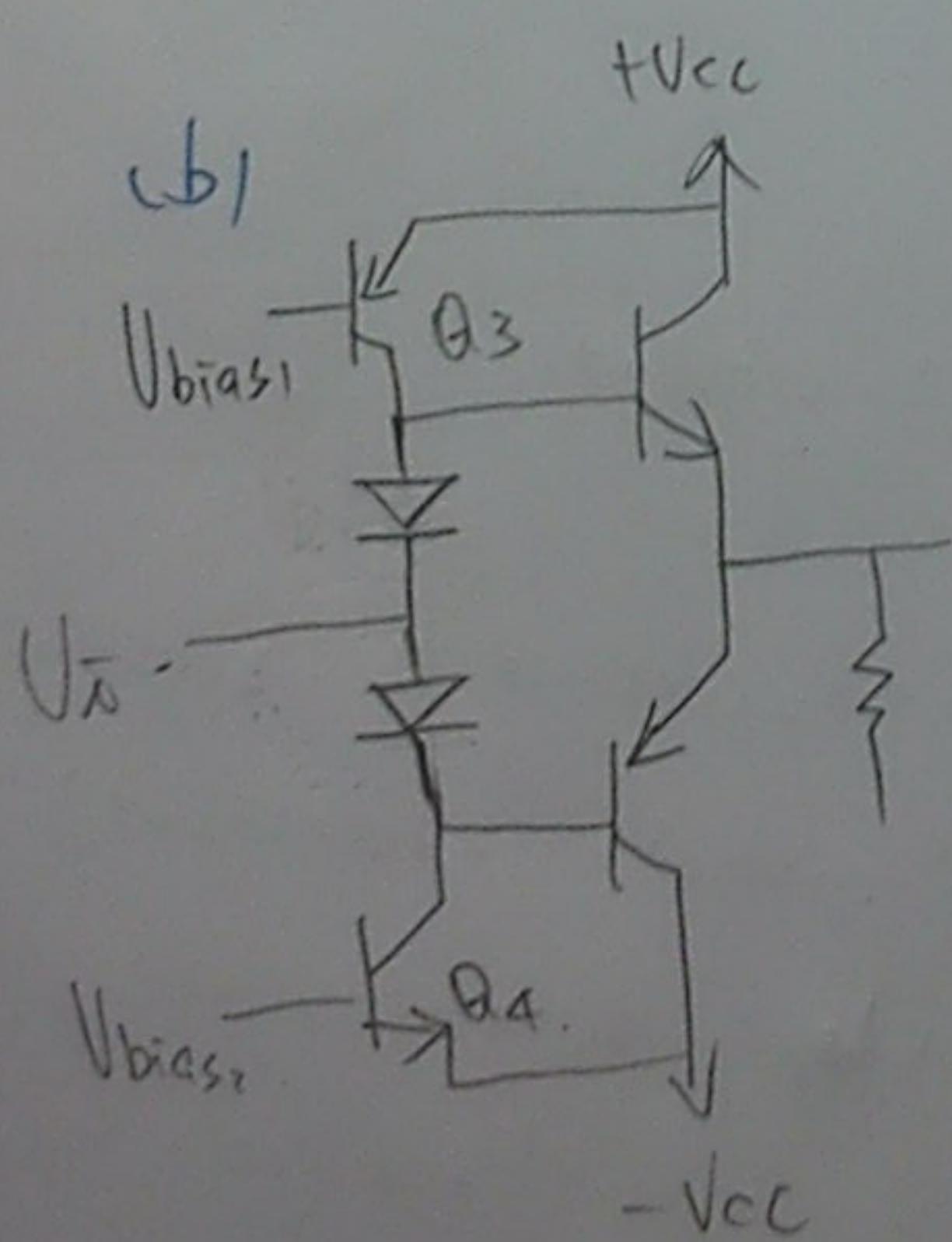\because Output 在 $(-V_{BE}) \sim V_{BE}$ 之間無放大 ($= 0$), 為死帶 dead band
故為 crossover distortion.



U_{bias1} 和 U_{bias2}

要使 Q_3 Q_4 持續有電流通過

12/15/2009

Mid - II.

MoonFox.



$$1.(a) I_{M1} = I_{REF} = k \cdot (V_{BS1} - V_t)^2 \Rightarrow V_{BS1} = V_t + \sqrt{\frac{I_{REF}}{k}}$$

$$I_{M2} = I_0 = k \cdot (V_{BS2} - V_t)^2 \Rightarrow V_{BS2} = V_t + \sqrt{\frac{I_0}{k}}$$

$$\therefore V_{BS1} = V_{BS2} + I_0 R$$

$$\Rightarrow \sqrt{\frac{I_{REF}}{k}} = \sqrt{\frac{I_0}{k}} + I_0 R$$

$$\sqrt{I_0} = \frac{\pm \sqrt{\frac{1}{k} + \sqrt{\frac{1}{k} + 4R\sqrt{\frac{I_{REF}}{k}}}}}{2R} = \frac{-1 + \sqrt{1 + 4RJK \cdot I_{REF}}}{2RK}$$

$$I_0 = \frac{1 - 2\sqrt{1 + 4RJK \cdot I_{REF}} + 1 + 4RJK \cdot I_{REF}}{4R^2 k}$$

$$= \frac{1 - \sqrt{1 + 4RJK \cdot I_{REF}} + 2R\sqrt{K \cdot I_{REF}}}{4R^2 k}$$

(b)

$$\frac{I_0}{I_{REF}} = \frac{I_s e^{\frac{V_{BE2}}{V_T}}}{I_s e^{\frac{V_{BE1}}{V_T}}} \Rightarrow I_0 = I_{REF} \cdot e^{\frac{V_{BE2} - V_{BE1}}{V_T}}$$

$$\therefore V_{BE1} = V_{BE2} + I_0 R \Rightarrow V_{BE2} - V_{BE1} = -I_0 R$$

$$\Rightarrow I_0 = I_{REF} e^{\frac{-I_0 R}{V_T}}$$

$$\ln \frac{I_0}{I_{REF}} = -\frac{I_0 R}{V_T}$$

$$\Rightarrow I_0 = -\frac{V_T}{R} \cdot \ln \frac{I_0}{I_{REF}} = -2.5 \times 10^{-6} \cdot \ln \frac{I_0}{10^{-3}}$$

$$\text{迭代法. 設 } I_0 = 10^{-5} \text{ A, } I_0 = -2.5 \times 10^{-6} \cdot \ln \frac{10^{-5}}{10^{-3}} = 1.15 \times 10^{-5}$$

$$\text{設 } I_0 = 1.15 \times 10^{-5}, \text{ 則 } I_0 = 1.116 \times 10^{-5}.$$

$$\text{設 } I_0 = 1.116 \times 10^{-5}, \text{ 則 } I_0 = 1.1238 \times 10^{-5}.$$

$$I_0 = 1.1238 \times 10^{-5}, \text{ 則 } I_0 = 1.1224 \times 10^{-5}.$$

$$\Rightarrow I_0 = 1.1224 \times 10^{-5} \text{ A}$$

$$= 11.224 \text{ mA.}$$

$$21.91. \quad I_R = \frac{0.6}{40k} = 15 \mu A.$$

設 $I_{C18} = x$.

$$\text{則 } I_{B18} = \frac{x}{200} \Rightarrow I_{E19} = I_R + I_{E18} = 15 \mu A + \frac{x}{200}$$

$$\therefore I_{E19} + I_{C18} = 180 \mu A.$$

$$15 + \frac{x}{200} + x = 180.$$

$$\frac{201}{200}x = 165, \quad x = 164.18 \mu A. \rightarrow I_{C18}.$$

$\because 0.6$ 是近似值.

$$\therefore \text{由數正確之 } V_{BE18} = V_T \times \ln \frac{I_{C18}}{I_S} = 0.588 \text{ (V)}$$

$$I_{C19} = 15.82 \mu A.$$

$$V_{BE19} = V_T \times \ln \frac{I_{C19}}{I_S} = 0.5295 \text{ (V)}.$$

$$\Rightarrow V_{BE14} + V_{EB20} = V_{BE19} + V_{BE18} = 1.1175.$$

$\because I_S \propto, I_C \propto$.

$$\therefore V_{BE14} = V_{EB20} = \frac{1.1175}{2} = 0.55875.$$

$$I_{C14} = I_S \cdot e^{\frac{V_{BE14}}{V_T}} = 3 \times 10^{-14} \times e^{\frac{0.55875}{0.025}} \\ = 1.526 \times 10^{-4} \text{ (A)}$$

(b).

$$V_{BE1} = V_T \times \ln \frac{I_{C1}}{I_S} = 0.5903. = V_{BE2}.$$

$$V_{BE1} + V_{BE2} = V_{BE14} + V_{EB20}.$$

$\because Q_{14}$ 和 $Q_{20} \gtrsim I_S \propto, I_C \propto$.

$$\therefore V_{BE14} = V_{EB20} = 0.5903.$$

$$I_{C14} = I_S \cdot e^{\frac{V_{BE14}}{V_T}} = 3 \times 10^{-14} \times e^{\frac{0.59034}{0.025}} \\ = 5.4 \times 10^{-4}.$$

(是 I_C 的 3 倍).

3.4.5.6 WTF!

01/12/2010

Final

Moon Fox.




1. > WTF


3. (A型)

$$(a) P_{out} = \frac{V_{rms}^2}{R} = \frac{1}{2} \times \frac{1}{T_{on}} = 0.32 \text{ W}$$

$$(b) I_A = 0.08$$

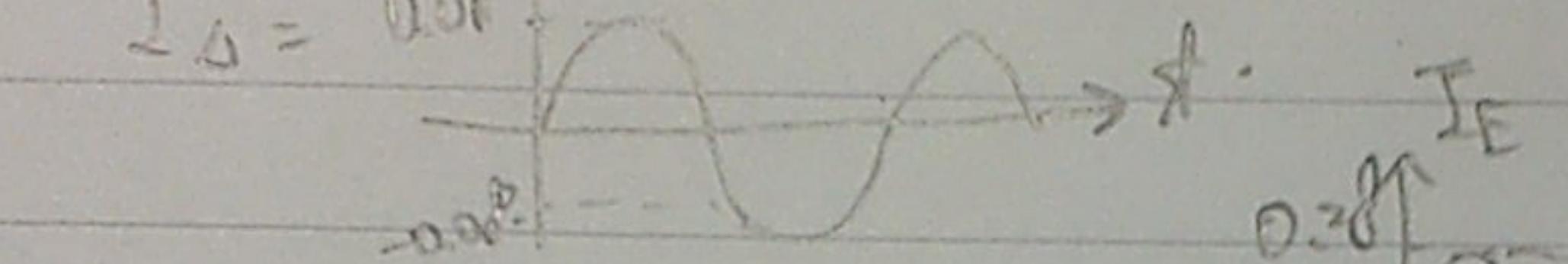
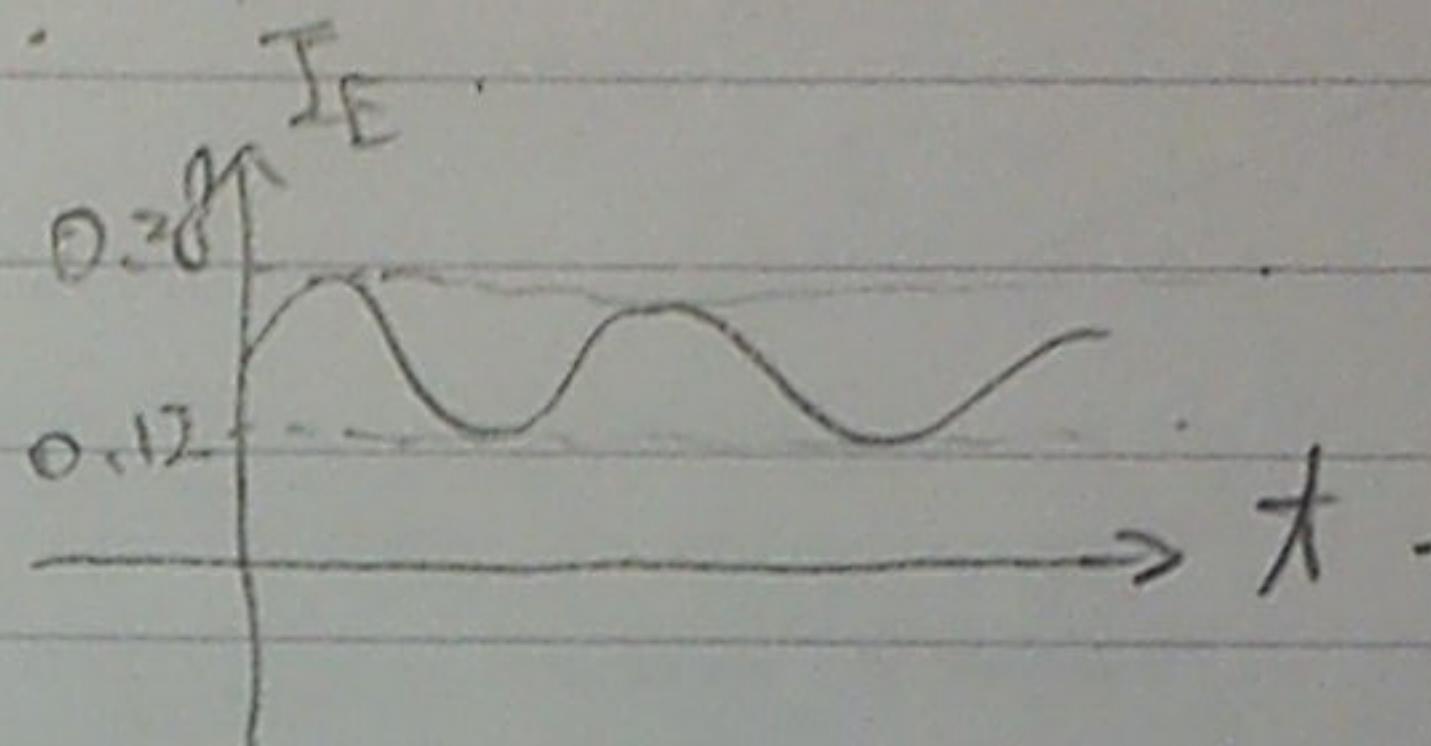
$$\Rightarrow I_{S1} = I_A + I_{bias} \Rightarrow$$



$$P_{in} = P_{A1} + P_{A2}$$

$$= I_{Eavg} \cdot V_{cc} + (-I_{bias})(-V_{cc}) \quad \left(\begin{array}{l} \text{忽略 Q}_3, R \text{ 的作用,} \\ \text{用 } I_{Eavg} \text{ 是因为 } V_{cc} \text{ 为定值} \end{array} \right)$$


$$= 0.2 \times 10 \times 2 = 4 \text{ W}$$

$$(c) \eta = \frac{P_{out}}{P_{in}} \times 100\%$$

$$= 8\%$$

4. (a)

$V_{in} - V_o$ 之圖

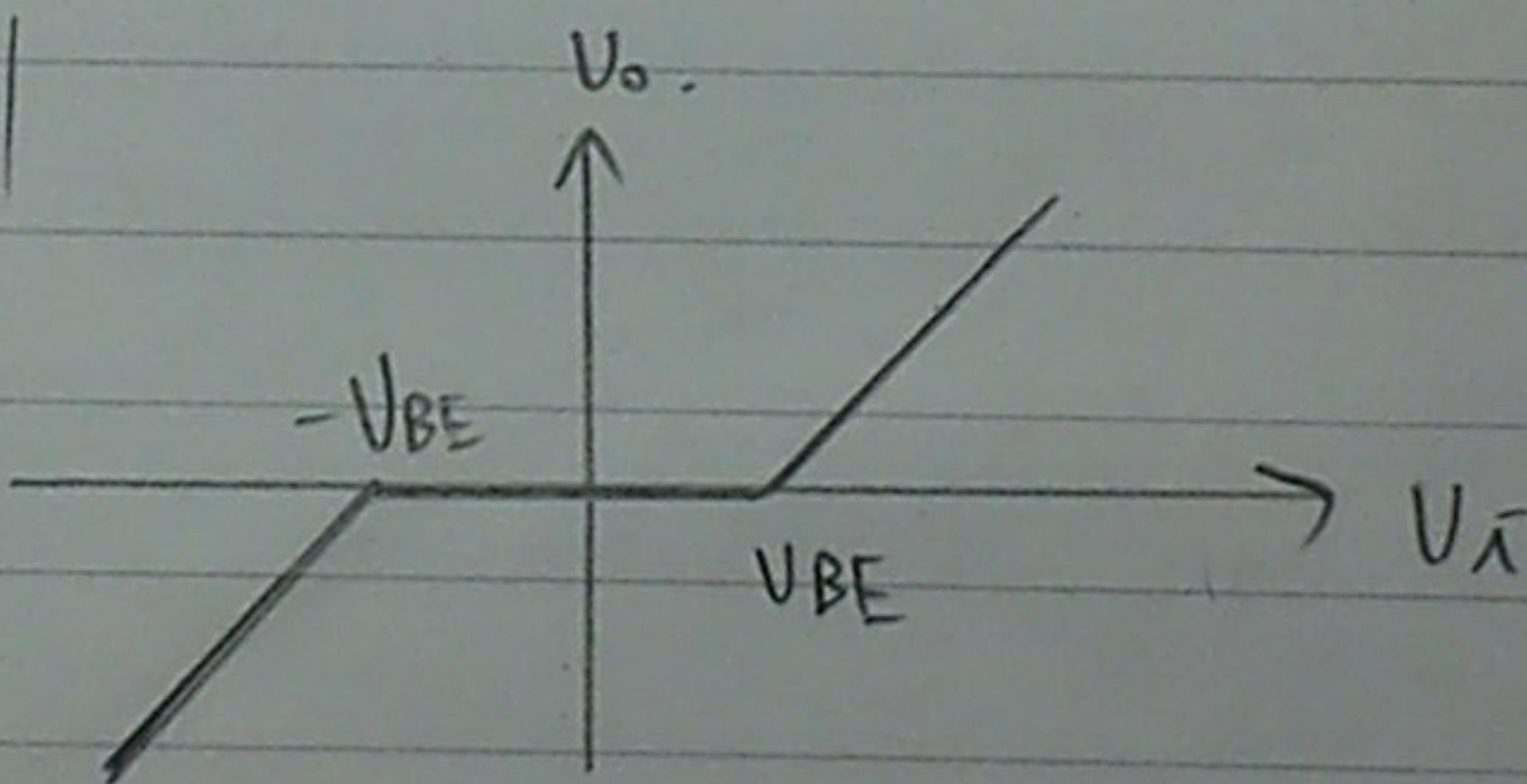


∴ Output 在 V_{in} 為 $(-V_{BE}) \sim V_{BE}$ 之間無放大 (為 0).

此區為死帶 dead band.

所以 V_o 不隨 V_{in} 做線性放大，為 crossover distortion

(b)

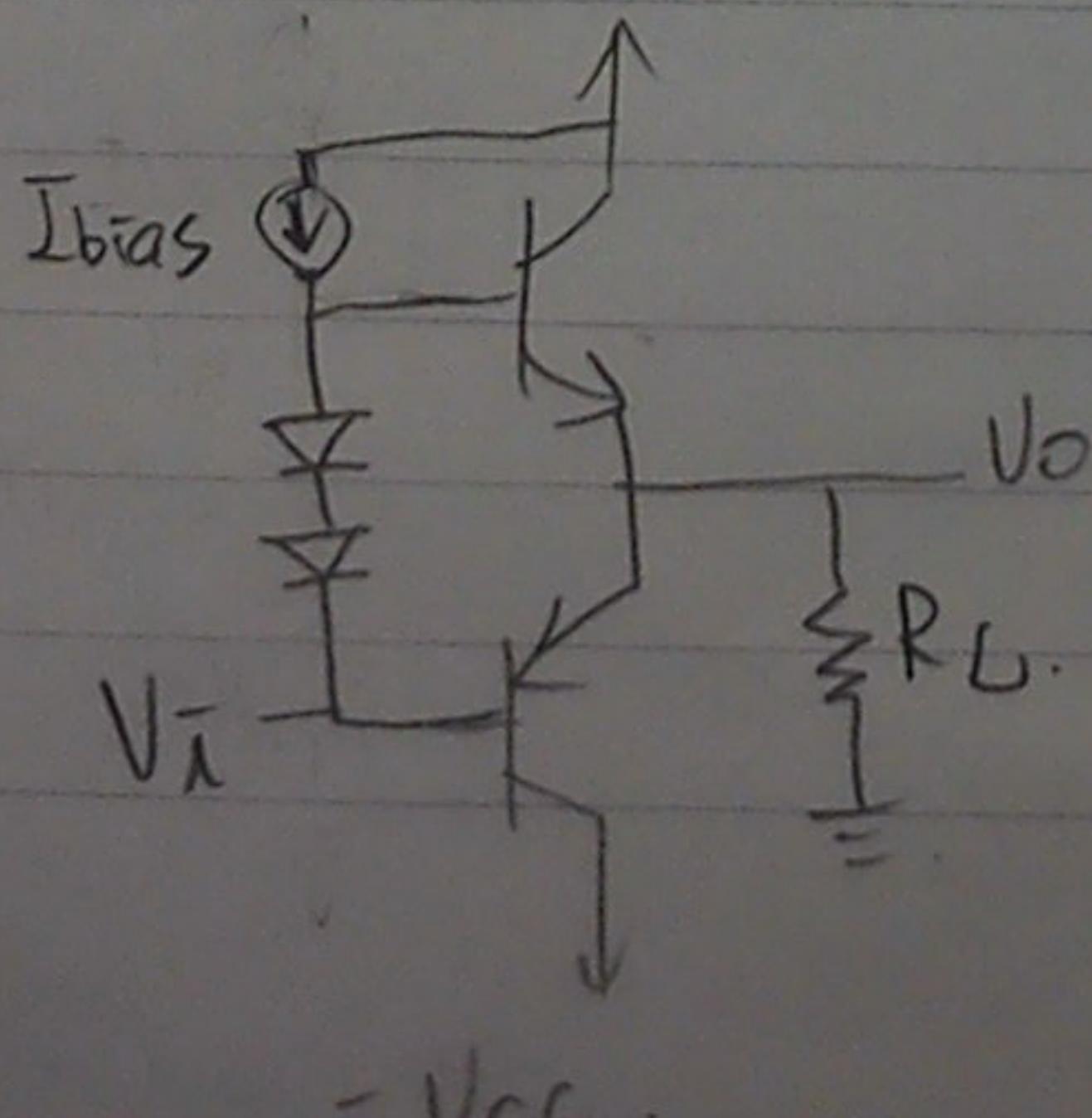

5. (a)

$$P_D = \frac{T_C - T_A}{\theta_{CS} + \theta_{SA}} = \frac{20}{0.7} = 100 \text{ (W)}$$

$$\Rightarrow T_S = T_A + P_D \cdot \theta_{SA} = 30 + 10 = 40^\circ C$$

(b) 100 (W)

$$(c) \theta_{SC} = \frac{T_S - T_C}{P_D} = \frac{50}{100 \text{ W}} = 0.5^\circ \text{C/W}$$

6. (a) If input $\bar{I}_A = I_0 \cos \omega t$ output $\bar{I}_o = I_0 + I_1 \cos \omega t + I_2 \cos(2\omega t) + I_3 \cos(3\omega t) \dots$ nth harmonic distortion $D_n = \left| \frac{I_n}{I_1} \right|, n = 2, 3, 4, \dots$

$$THD = \sqrt{D_2^2 + D_3^2 + D_4^2} \dots$$


If input $\bar{I}_A = I_a (\cos \omega_1 t + \cos \omega_2 t)$

$$\begin{aligned} \text{output } \bar{I}_o &= G(\bar{I}_A)^2 = G I_a^2 [\cos^2(\omega_1 t) + 2 \cos(\omega_1 t) \cos(\omega_2 t) + \cos^2(\omega_2 t)] \\ &= G I_a^2 \left[\frac{1}{2} + \frac{1}{2} \cos(2\omega_1 t) + \cos[(\omega_1 + \omega_2)t] + \cos[(\omega_1 - \omega_2)t] \right. \\ &\quad \left. + \frac{1}{2} + \frac{1}{2} \cos(2\omega_2 t) \right]. \end{aligned}$$

 \Rightarrow 頻率有 $\omega_1, \omega_2, 2\omega_1, 2\omega_2, \omega_1 + \omega_2, \omega_1 - \omega_2$

inter-modulation distortion

(有非原頻率之整數倍的即是)

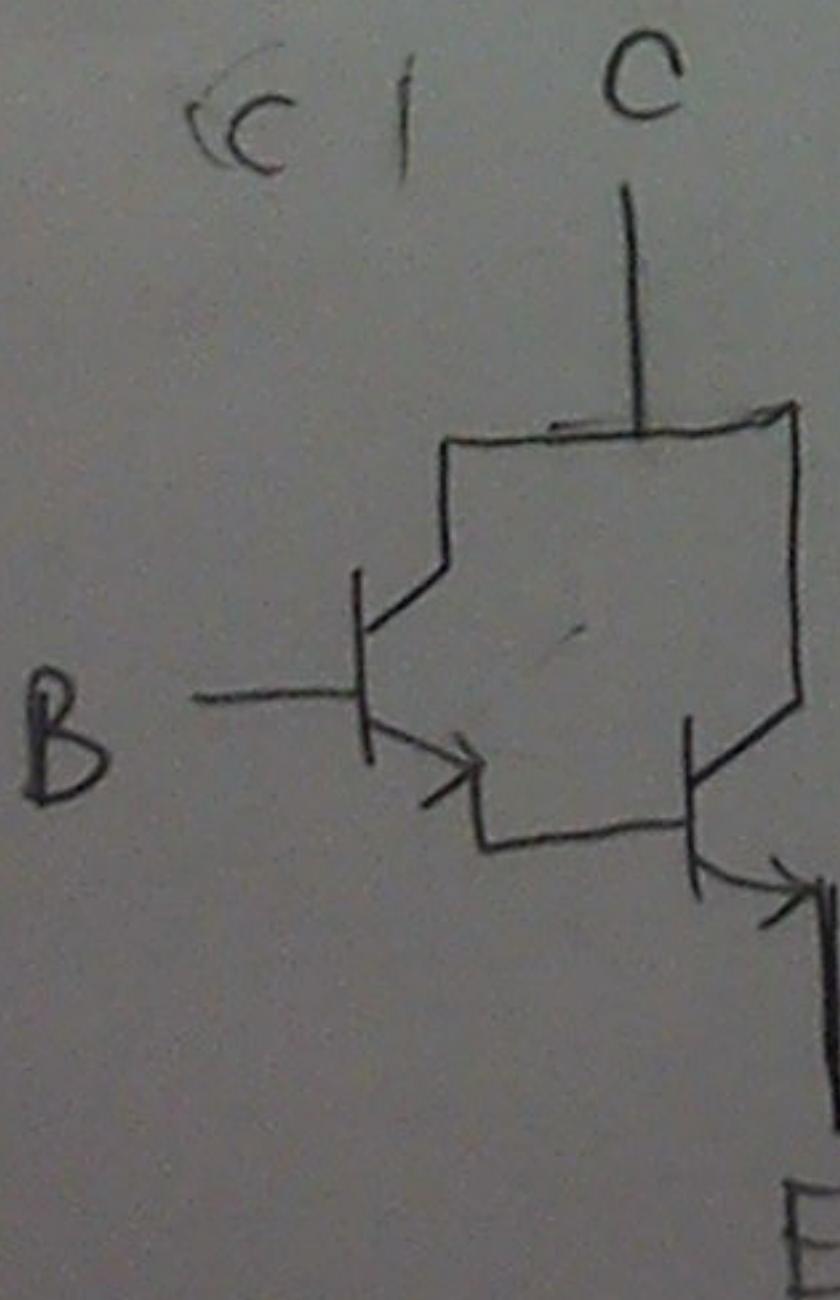

用 2 個 BJT 合成的 BJT.

电流放大倍率更高!!

但 V_{BE} 為原本的 2 倍

2010 / 12 / 07



1. (a) $I_{C19} = \frac{V_{BE18}}{R_{10}} = 15 \text{ mA}$

$I_{C19} = I_S \cdot e^{\frac{V_{BE}}{V_T}}$ (設 β 很大, 所有 $I_B \approx 0$).

$$\Rightarrow V_{BE} = V_T \ln\left(\frac{I_{C19}}{I_S}\right) = 0.025 \times \ln\left(\frac{15 \text{ mA}}{10^{-14}}\right) = 0.528 \text{ (V)}$$

$V_{BE14} + V_{EB20} = V_{BE19} + V_{BE18} = 1.128$

$$\Rightarrow V_T \ln\frac{I_{C14}}{I_S} + V_T \ln\frac{I_{C20}}{I_S} = 1.128$$

$$\Rightarrow I_{C14} = I_S \cdot e^{\frac{V_{BE14}}{V_T}} = 3 \times 10^{-14} \times e^{\frac{0.564}{0.025}} = 18.83 \text{ mA}$$

$I_{C18} = 280 \mu\text{A} - 15 \mu\text{A} = 265 \mu\text{A}$

(b)

$$V_{BE25} = V_T \times \ln\frac{I_{C25}}{I_S} = 0.025 \times \ln\frac{280 \mu\text{A}}{10^{-14}} = 0.6014 \text{ (V)}$$


$$I_{C19} = I_S \cdot e^{\frac{V_{BE14}}{V_T}} = 3 \times 10^{-14} \times e^{\frac{0.6014}{0.025}} = 8.4 \times 10^{-9} \text{ (A)}$$

2. WTF

3. WTF^2 .

4. WTF^3 .

5. (a)

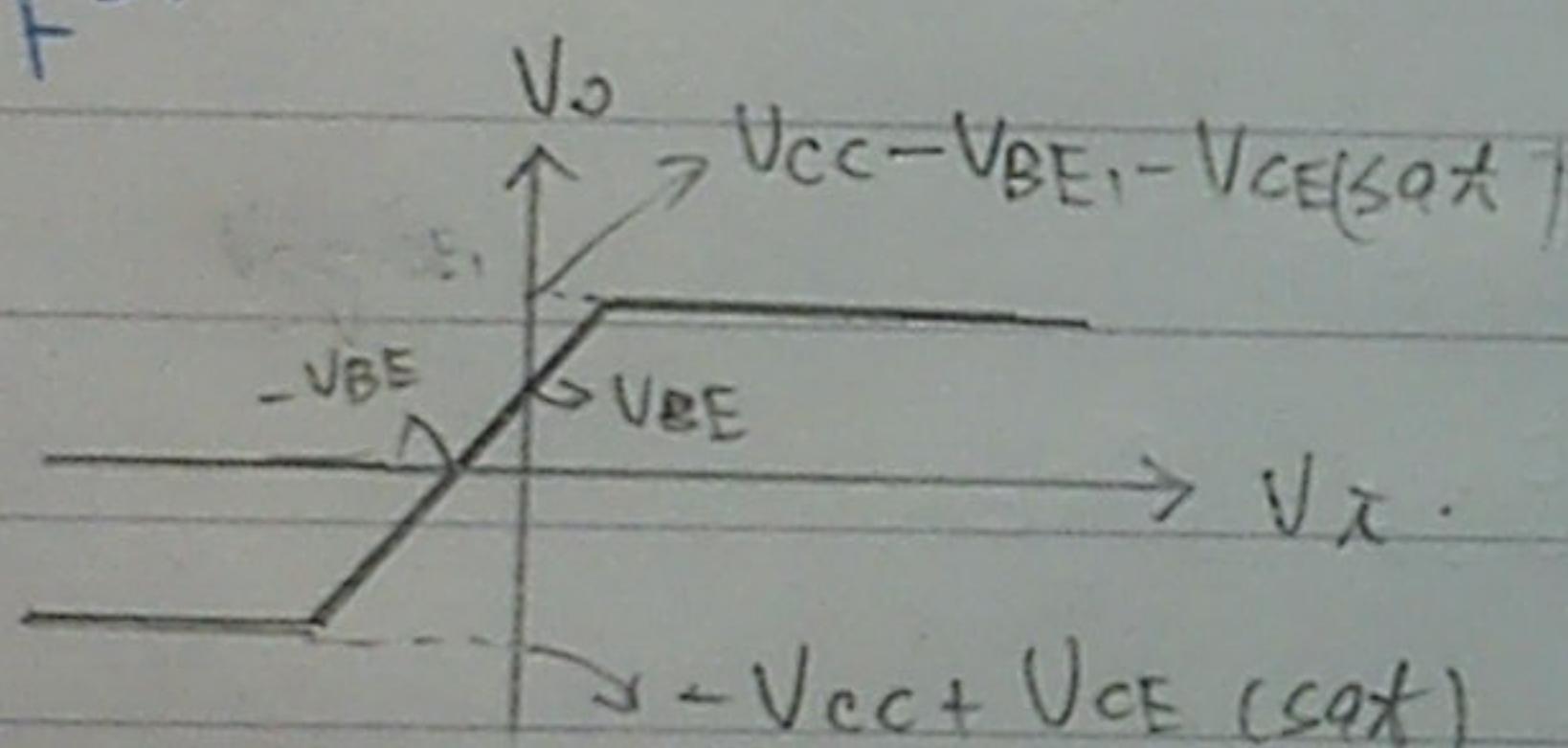

(b) 減少 crossover distortion

(c) input = $\bar{i}_i = I_i \cos \omega t$

$$\text{output } \bar{i}_o = I_o + I_1 \cos \omega t + I_2 \cos(2\omega t) + I_3 \cos(3\omega t) + \dots$$

$$\text{Nth. harmonic distortion } D_N = \left| \frac{I_N}{I_1} \right|, \quad N = 2, 3, 4, \dots$$

$$THD = \sqrt{D_2^2 + D_3^2 + D_4^2 + \dots}$$

(d) if $\bar{i}_N = I_o + I_1 \cos \omega t + I_2 \cos(2\omega t) + I_3 \cos(3\omega t) + I_4 \cos(4\omega t)$

$$\therefore \bar{i}_P(\omega t) = \bar{i}_N(\omega t + \pi)$$

$$\bar{i}_P = I_o - I_1 \cos \omega t + I_2 \cos 2\omega t - I_3 \cos 3\omega t + I_4 \cos 4\omega t$$


$$\bar{i}_o = \bar{i}_N - \bar{i}_P = 2 I_1 \cos \omega t + 2 I_3 \cos 3\omega t + \dots$$

\Rightarrow even-order harmonics are eliminated.

8.19 | Thermal Resistance, 代表一物体阻止熱流通過的能力。

公式為 $\frac{\text{物体之面溫度差}}{\text{流逝的功率}}$


$P_D(\max)$.

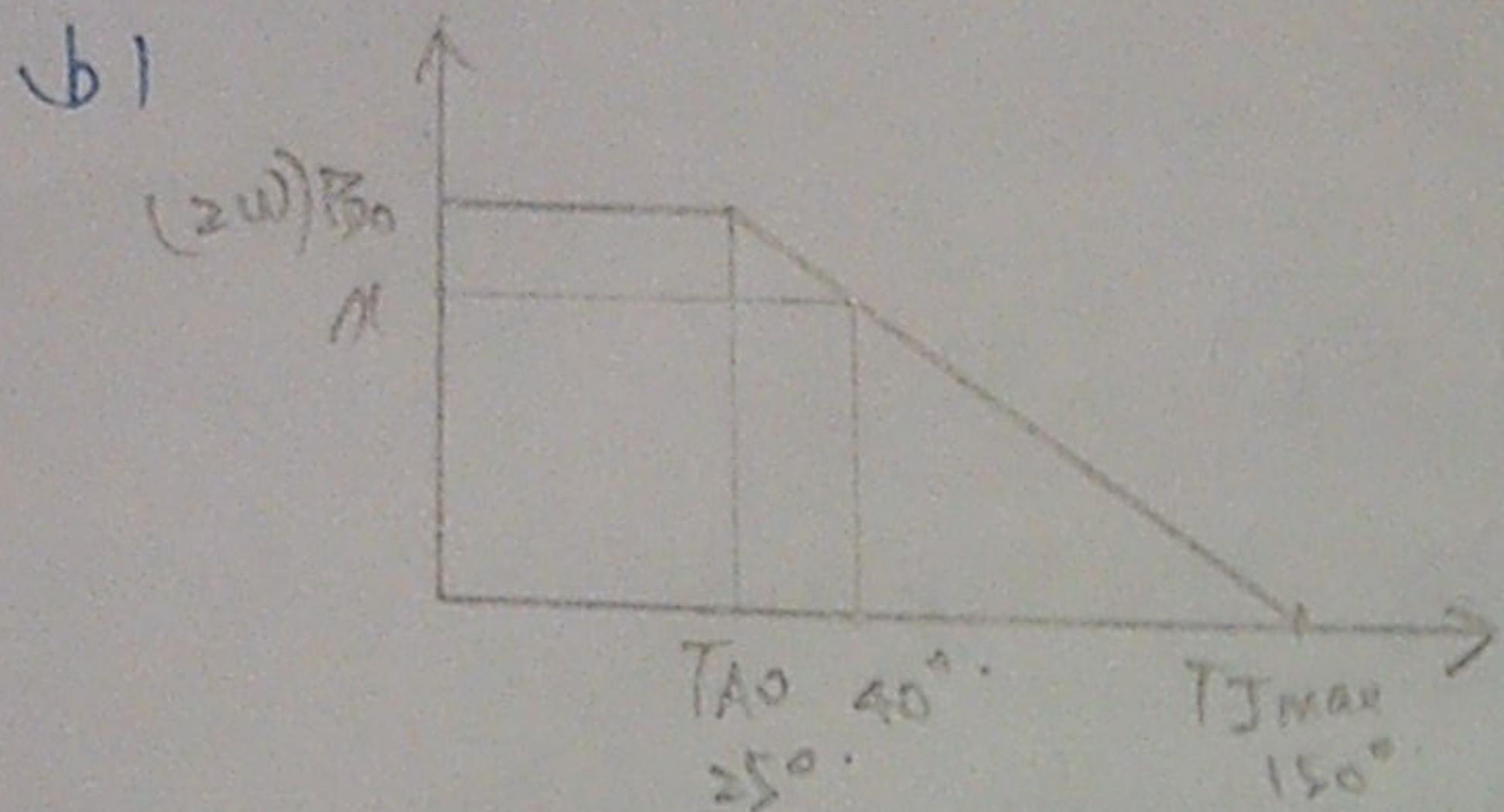

$$X = 1.76(\omega)$$

||

c1.

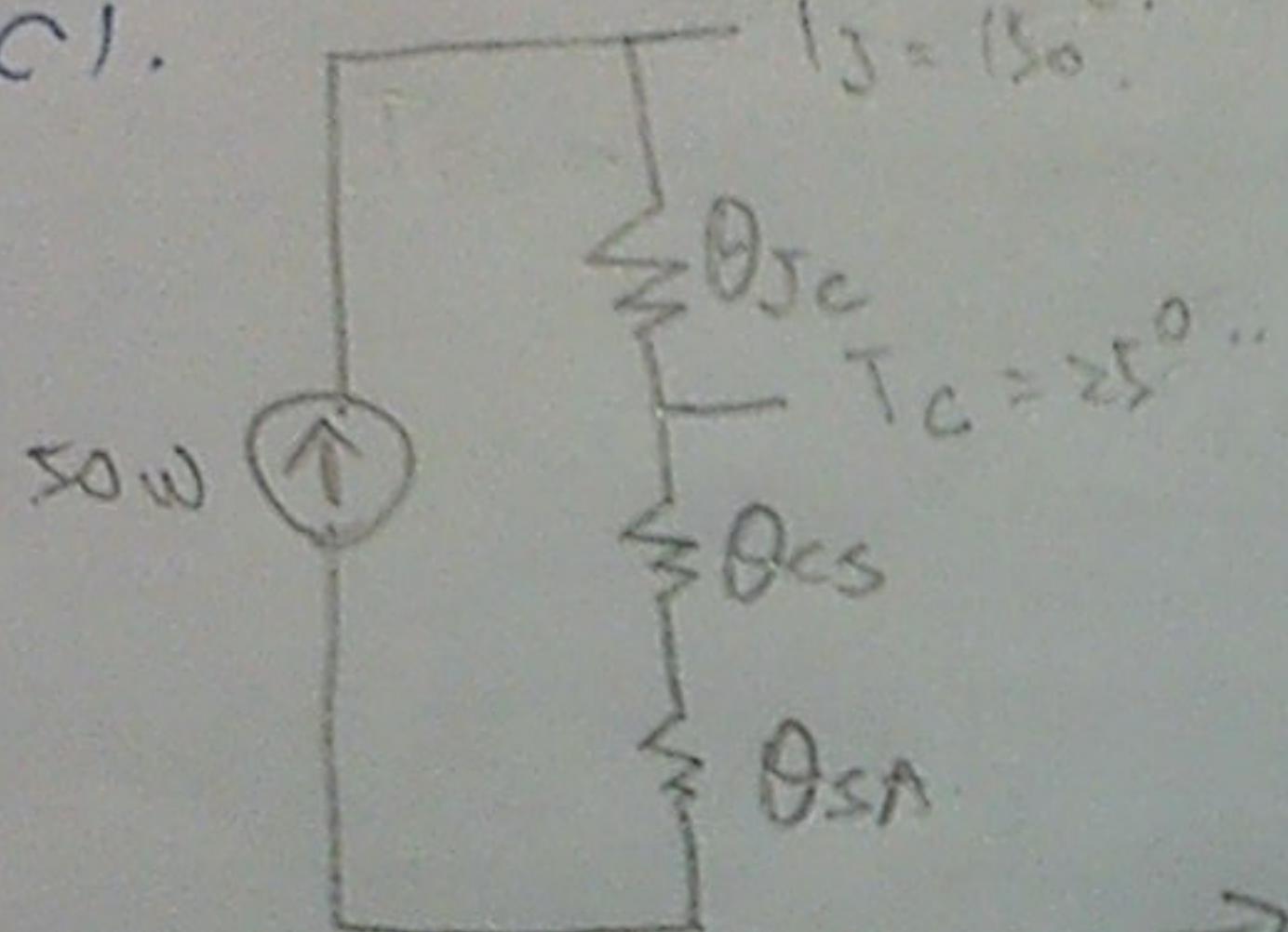

$$\theta_{JC} = \frac{150^\circ - 25^\circ}{50} = 2.5^\circ C/W$$

$$\Rightarrow \theta_{JA} = \theta_{JC} + \theta_{CS} + \theta_{SA} = 2.5 + 0.5 + 5 = 8^\circ C/W$$

$$P_{D\max} = \frac{T_{J\max} - T_A}{\theta_{JA}} = \frac{150 - 40}{8} = 13.75 (\omega)$$

||

D1

The infinite heat sink $\Rightarrow \theta_{CA} = 0$.

$$\Rightarrow \theta_{JA} = \theta_{JC}$$

$$P_{D\max} = \frac{150 - 50}{2.5} = 40 (\omega)$$

||