

系級班別：\_\_\_\_\_ 學號：\_\_\_\_\_ 姓名：\_\_\_\_\_

(不可攜帶資料，可用計算機) 請在答案卷右上方畫上成績欄，謝謝。

(20%) 1. A tuned-amplifier is shown in Fig. p1.

(a) Please show its small-signal equivalent circuit including the FET output resistance  $r_o$  and output capacitance  $C_o$ . (8%)

(b) Derive the (i) voltage gain  $\frac{V_o(s)}{V_i(s)}$ , (ii) center frequency  $\omega_0$ , (iii) 3-dB bandwidth B, and (iv) Q factor.

(12%)

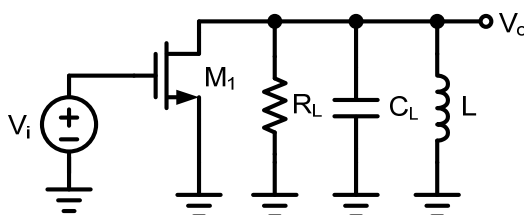


Fig. p1

(20%) 2. For Fig. p2(a) and Fig. p2(b), their maximum  $V_o$  is  $L_+$  and minimum  $V_o$  is  $L_-$ .

(a) Draw their transfer characteristics of  $V_o$  vs.  $V_i$ . (10%)

(b) Calculate their negative and positive threshold voltages ( $V_{TL}$  and  $V_{TH}$ ) of input triggers. (10%)

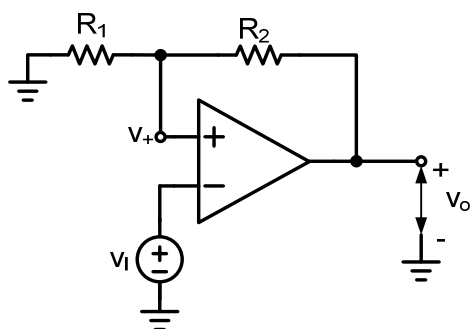


Fig. p2(a)

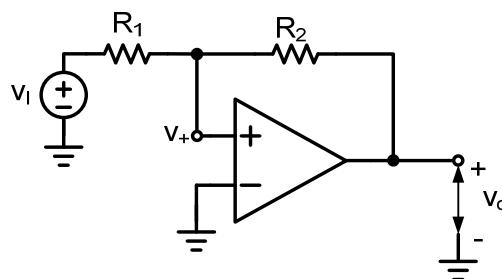


Fig. p2(b)

(20%) 3. For the circuit in Fig. p3, let the OPAMP saturation voltage be  $\pm 10V$ ,  $R_1 = 100k\Omega$ ,  $R_2 = R = 1M\Omega$ , and  $C = 0.01\mu F$ . Please draw the detailed waveforms of various nodes and derive the oscillation frequency of the circuit.

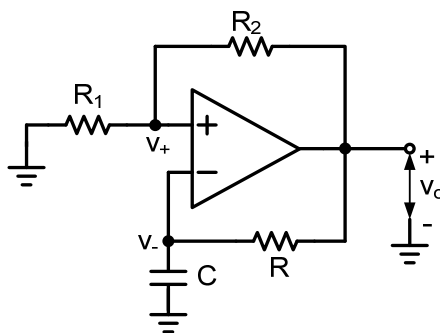


Fig. p3

- (30%) 4. (a) Briefly explain total harmonic distortion. (3%)  
(b) Briefly explain intermodulation distortion. (3%)  
(c) Briefly explain a (i) class A, (ii) class B, and (iii) class AB amplifier. (12%)  
(d) Demonstrate that even harmonics are eliminated in a balanced push-pull amplifier. (2%)  
(e) Show that the maximum conversion efficiency of idealized class B push-pull circuit is 78.5 percent. (10%)
- (20%) 5. For a class B output stage shown in Fig. p5,  
(a) Explain its crossover distortion.  
(b) Give an example for reducing its crossover distortion.

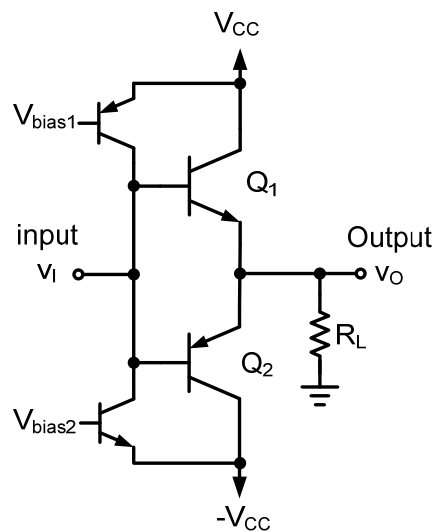


Fig. p5