

系級班別：\_\_\_\_\_ 學號：\_\_\_\_\_ 姓名：\_\_\_\_\_

(不可攜帶資料，可用計算機) 請在答案卷右上方畫上成績欄，謝謝。

(10%) 1. Derive the normalized polynomial of a 2<sup>nd</sup>-order Butterworth filter with  $\varepsilon = 1$ .

$$\text{(Butterworth transmission function} = \frac{1}{\sqrt{1 + \varepsilon^2 \left(\frac{\omega}{\omega_p}\right)^{2N}}})$$

(10%) 2. Find the Butterworth transfer function that meets the following low-pass filter specification:  $f_p=10$ -kHz,  $f_s=15$ -KHz,  $A_{\min}=10$ dB, dc gain=1 and  $\varepsilon=1$ .

(20%) 3. Your answers should be as simple as possible.

(a) Plot the rough transmission characteristics of Fig. 3. (10%)

(b) Determine the order (5%)

(c) Show its approximate transfer function. (5%)

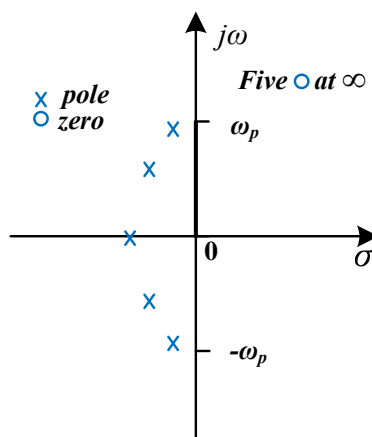


Fig. 3

(20%) 4. (a) Derive a block diagram of a two-integrator-loop biquad. (10%)

(b) Circuit implementation of (a) with KHN biquad. (10%)

(10%) 5. For a Antoniou inductance-simulation circuit.

(a) Briefly explain its purpose. (5%)

(b) Show its application for a 2<sup>nd</sup>-order LPF. (5%)

(20%) 6. For a dc voltage of 1V applied to the input of the circuit of Fig. 6, in which  $C_1$  is 1pF.

- What charge is transferred for each cycle of the two-phase clock? (3%)
- For a 100-kHz clock, what is the average current drawn from the input source. (4%)
- For a feedback capacitance  $C_2$  of 10pF, what change in the output for each cycle of the clock? (3%)
- Why is the time constant of the circuit in Fig. 6 accurate? (10%)

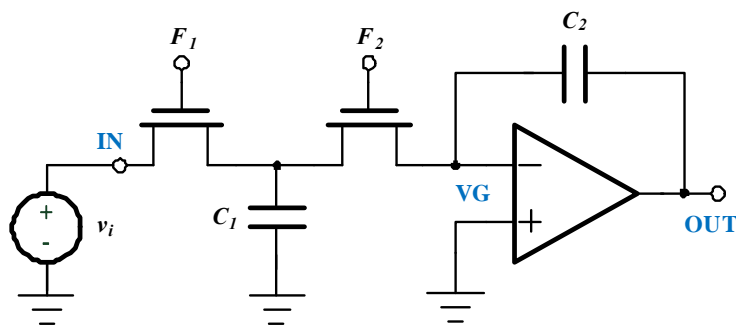


Fig. 6

(10%) 7. It is required to design a tuned amplifier of the type shown in Fig. 7, having  $f_0=1\text{MHz}$ , 3-dB bandwidth = 10-kHz, and center-frequency gain=-10V/V. The FET available has at the bias point  $g_m=5\text{mA/V}$  and  $r_o=10\text{k}\Omega$ . The output capacitance is negligibly small. Determine the values of  $R_L$ ,  $C_L$ , and  $L$ .

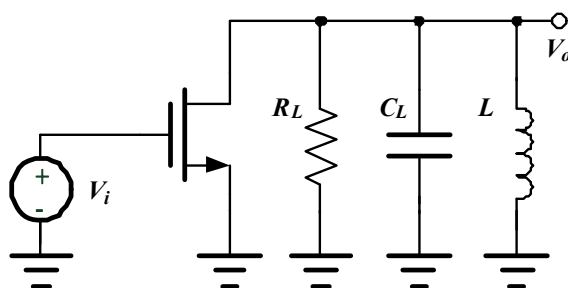


Fig. 7

(10%) 8. For the circuit in Fig. 8, find its oscillation frequency.

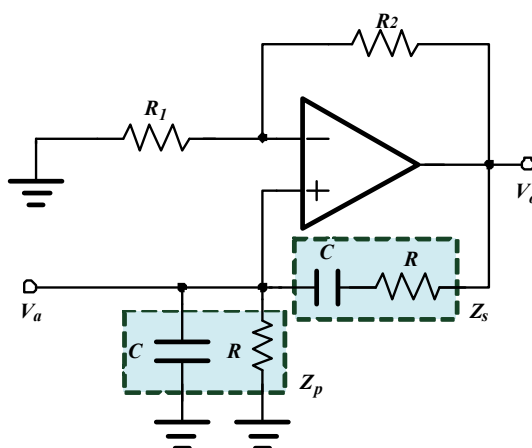


Fig. 8