 


(20%) 1. Figs. P1(a) and P1(b) are two different types of output stage in the 741 op-amp circuit without the protection circuitry. Assume $V_T = 25\text{mV}$, $I_S = 3 \times 10^{-14}\text{A}$ for Q_{14} and Q_{20} , $I_S = 10^{-14}\text{A}$ for the other BJTs, $R_{10} = 40\text{k}\Omega$, and $I_{C13A} = 280\mu\text{A}$. Neglect the base currents of all BJTs.

(a) In Fig. P1(a), if V_{BE18} is found to be 0.6V iteratively, find I_{C14} , I_{C18} , and I_{C19} . **(10%)**

(b) In Fig. P1(b), if Q_{25} and Q_{26} are used to establish the voltage drop between the bases of Q_{14} and Q_{20} , find I_{C14} . **(10%)**




(20%) 2. Fig. P2 shows a 3-bit DAC using R-2R resistor ladder network. Given $V_{REF} = 1.8\text{V}$, and $R = 10\text{k}\Omega$,

(a) If bits $B_2B_1B_0 = (100)_2$, find v_X . **(5%)**

(b) If bits $B_2B_1B_0 = (010)_2$, find v_X . **(5%)**



(c) If bits $B_2B_1B_0 = (001)_2$, find v_X . **(5%)**

 (d) Derive $\frac{v_O}{V_{REF}}$ in terms of B_0 , B_1 , B_2 , R_1 , and R_2 . **(5%)**



(10%) 3. Figs. P3(a) and P3(b) show a 3-bit charge-redistribution ADC, which is operating at hold phase and charge-redistribution phase, respectively.

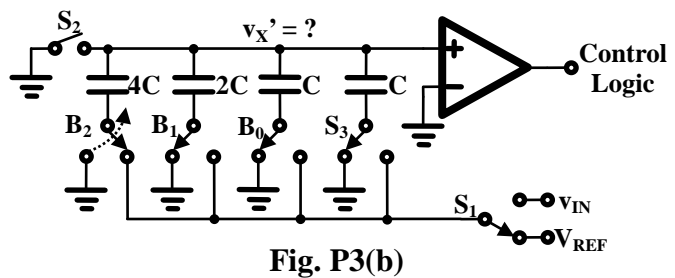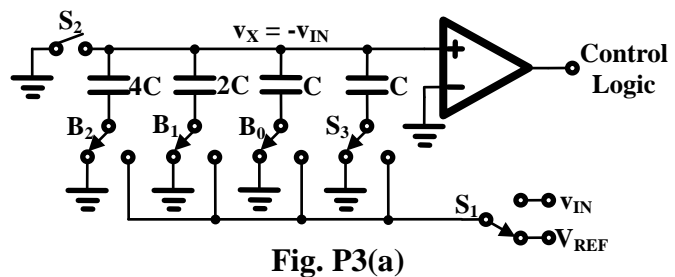In Fig. P3(a), switches B_0 through B_2 are connected to GND. Then, switch B_2 is suddenly connected to V_{REF} , as shown in Fig. P3(b). Assume $V_{REF} = 1.8\text{V}$ and $v_{IN} = 1.2\text{V}$. Find the voltage v_X' in Fig. P3(b).



- (10%) 4. Fig. P4 shows a 14-bit dual-slope ADC. Assume $C = 100\text{pF}$, $V_{\text{REF}} = -1.8\text{V}$, and v_{IN} is in the range of 0V and 1.8V . If the maximum conversion time T is 1ms , find the value of R and the required clock frequency f_{clk} . ($f_{\text{clk}} = 1 / T_{\text{clk}}$)

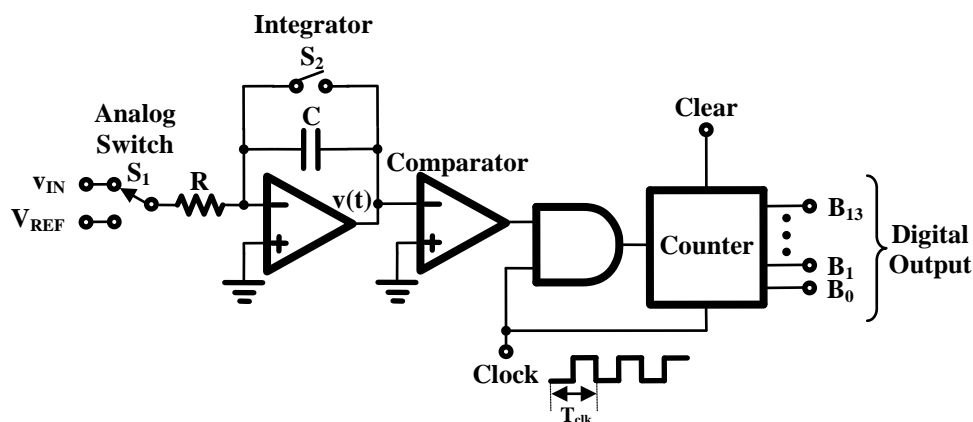


Fig. P4

- (20%) 5. Fig. P5 shows a class AB push-pull amplifier.

- Sketch its transfer characteristic v_O vs. v_{IN} . (5%)
- Briefly explain the benefit of adding the two diodes D_1 and D_2 . (5%)
- Briefly explain “total harmonic distortion.” (5%)
- Show that for matched devices Q_N and Q_P , the even-order harmonics at v_O are eliminated. (5%)

 


Fig. P5

- (20%) 6. A power BJT is specified to have maximum junction temperature T_{Jmax} of 150°C . Assume the maximum power dissipation is to be derated linearly above 25°C .
- Briefly explain “thermal resistance.” (5%)
 - Assume this transistor has a maximum power dissipation P_{D0} of 2W at an ambient temperature T_{A0} of 25°C . Find the maximum power P_{Dmax} that can be dissipated safely by this transistor **in free air (with no special arrangements for cooling)** at an ambient temperature $T_{\text{A}} = 40^\circ\text{C}$. (5%)
 - Assume this transistor has a maximum power dissipation $P_{\text{Dmax}}(T_{\text{C0}})$ of 50W at a case temperature T_{C0} of 25°C , and a heat sink is utilized. The thermal resistance θ_{CS} , between case and heat sink, is 0.5°C/W . θ_{SA} , between heat sink and ambience, is 5°C/W . Find the maximum power P_{Dmax} that can be dissipated safely by this transistor at $T_{\text{A}} = 50^\circ\text{C}$. (5%)
 - Referring to (c), find the maximum power P_{Dmax} that can be dissipated safely by this transistor **with an infinite heat sink** at $T_{\text{A}} = 50^\circ\text{C}$. (5%)