

(20%) 1. Figs. 1(a) and 1(b) show a basic current source and Widlar current source, respectively. Assume that  $V_{BE}$  is 0.7V at a current of 1mA, the thermal voltage  $V_T=25\text{mV}$ ,  $V_{CC}=10\text{V}$ , and neglect the effect of finite  $\beta$ .

**To generate a current  $I_O=10\mu\text{A}$ ,**

(a) find  $R_1$  in Fig. 1(a). (5%)

(b) for Fig. 1(b), if  $I_{REF}=1\text{mA}$ , find  $R_2$  and  $R_3$ .

(10%)

(c) explain the advantage of Widlar current source.

(5%)

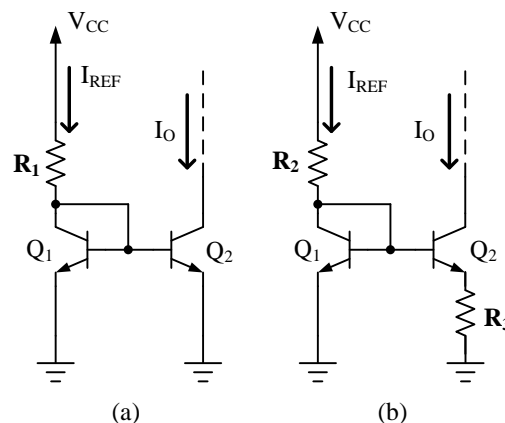


Fig. 1

(15%) 2. Figs. 2(a) and 2(b) show two different types of output stage, respectively. Assume that  $V_T=25\text{mV}$ ,  $I_S=3\times 10^{-14}\text{A}$  for  $Q_{14}$  and  $Q_{20}$ , while  $I_S=10^{-14}\text{A}$  for the other BJTs,  $R_{10}=40\text{k}\Omega$ , and  $I_{C13A}=280\mu\text{A}$ . Neglect the base currents of all BJTs.

(a) In Fig. 2(a), if  $V_{BE18}$  is found to be 0.6V iteratively, find  $I_{C18}$ ,  $I_{C19}$ , and  $I_{C20}$ . (10%)

(b) In Fig. 2(b), if  $Q_{25}$  and  $Q_{26}$  are used to establish the voltage drop between the bases of  $Q_{14}$  and  $Q_{20}$ , find  $I_{C14}$ . (5%)

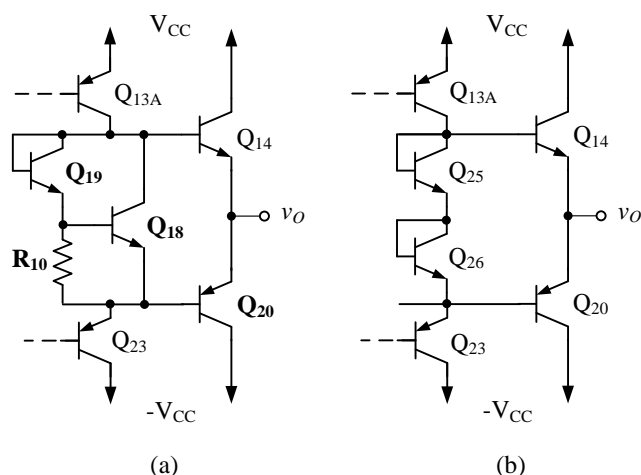


Fig. 2

(15%) 3. Please give definitions of the following terms.

(a) slew rate (5%)

(b) inter-modulation distortion (5%)

(c) total harmonic distortion (5%)

(20%) 4. For a class-B output stage in Fig. 4, let dual-supply voltage  $V_{CC}=10\text{V}$  and  $R_L=8\Omega$ . If the output  $v_O$  is an **8-V-peak** sinusoid.

(a) Neglecting the crossover distortion, please find the **average power delivered to the load  $R_L$** , the **average power drawn from the supplies**, and the **power-conversion efficiency  $\eta$** . (15%)

(b) Please explain the crossover distortion for the output stage in Fig. 4 (5%)

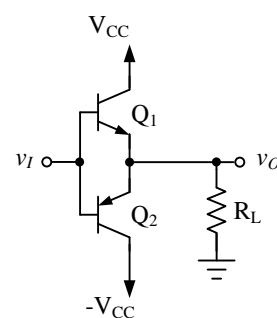


Fig. 4

- (15%) 5. Figs. 5(a) and 5(b) show two different types of CMOS class AB output stage, respectively. Assume  $|V_{OV}|=0.2V$  for all transistors,  $|V_{tp}|=0.8V$ ,  $V_{tn}=0.7V$ , and dual-supply voltage  $V_{CC}=2.5V$ .
- (a) Fig. 5(a) shows a class AB utilizing source followers  $Q_1$  and  $Q_2$ , please find the **output swing range of  $v_O$**  (5%)
- (b) Fig. 5(b) shows a class AB utilizing common-source transistors  $Q_5$  and  $Q_6$ , please find the **output swing range of  $v_O$**  (5%)
- (c) Please **draw** a modified output stage to reduce the output resistance of Fig. 5(b) **by using feedback**. Briefly explain your reason. (5%)

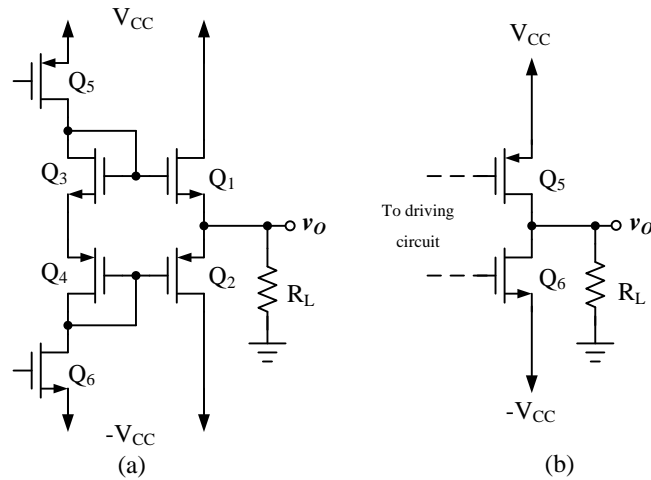


Fig. 5

- (15%) 6. When a power transistor is operated at junction temperature  $T_J$  of  $150^\circ\text{C}$  with a heat sink, the case temperature  $T_C$  is found to be  $120^\circ\text{C}$ . The case is attached to the heat sink with a bond having a thermal resistance  $\theta_{CS}=0.7^\circ\text{C/W}$  and the thermal resistance of the heat sink  $\theta_{SA}=0.2^\circ\text{C/W}$ , as shown in Fig. 6. If the ambient temperature  $T_A$  is  $30^\circ\text{C}$ , please calculate
- (a) heat sink temperature  $T_S$ . (5%)
- (b) power dissipated in the device  $P_D$ . (5%)
- (c) thermal resistance from junction to case,  $\theta_{JC}$ . (5%)

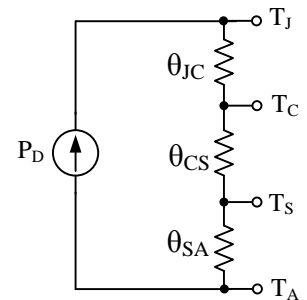


Fig. 6