

(15%) 1. Consider a filter function whose poles and zeros are plotted in s-plane shown in **Fig. P1**. Please specify

(a) which type of filters it is. (low-pass/ high-pass/ band-pass/ all-pass)

Explain your reason. (10%)

(b) its filter order N. Explain your reason. (5%)

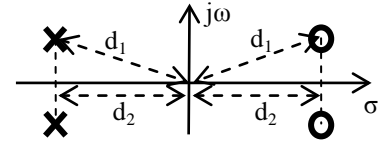


Fig. P1

(20%) 2. Consider an N^{th} -order Butterworth low-pass filter whose maximum allowed variation in passband is A_{max} , minimum required stopband attenuation is A_{min} , passband edge is ω_p , and stopband edge is ω_s . Find the required filter orders to meet the following specifications, respectively.

(Butterworth magnitude function = $\frac{1}{\sqrt{1 + \varepsilon^2 \left(\frac{\omega}{\omega_p}\right)^{2N}}}$)

(a) $A_{\text{max}} = 1\text{dB}$, $A_{\text{min}} = 50\text{dB}$, $\omega_p = 100\text{kHz}$, and $\omega_s = 1\text{MHz}$. (10%)

(b) $A_{\text{max}} = 1\text{dB}$, $A_{\text{min}} = 50\text{dB}$, $\omega_p = 100\text{kHz}$, and $\omega_s = 200\text{kHz}$. (10%)

(15%) 3. **Fig. P3** shows a switched-capacitor integrator and its two-phase clock.

(a) Express the equivalent time-constant for the integrator in terms of C_1 , C_2 , and T_c . (5%)

(b) Compared with an active-RC integrator, what are the benefits of a switched-capacitor integrator for on-chip implementation? (5%)

(c) Explain how stray capacitances affect the circuit. (5%)

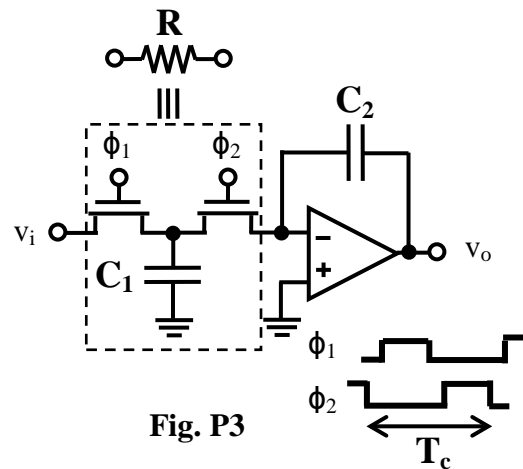


Fig. P3

(15%) 4. (a) Please describe the Barkhausen criterion. (10%)

(b) In **Fig. P4**, will the circuit start oscillation or not? Why? (5%)

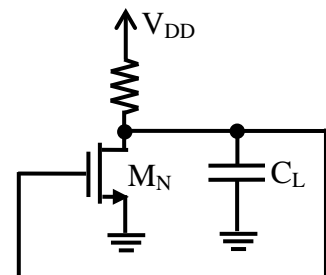


Fig. P4

(20%) 5. **Fig. P5a** and **Fig. P5b** are bistable circuits with inverting and non-inverting topologies, respectively. Both have output saturation voltages $L_+ = -L_- = 12\text{V}$, and the threshold voltages $V_{TH} = -V_{TL} = 4\text{V}$.

(a) Please sketch the transfer characteristic curves of both inverting and non-inverting topologies, respectively (mark the L_+ , L_- , V_{TH} , V_{TL} , and the direction of the transfer operation on your plots). (10%)

(b) Let $R_1 = 10\text{k}\Omega$, please find R_2 and R_3 . (10%)

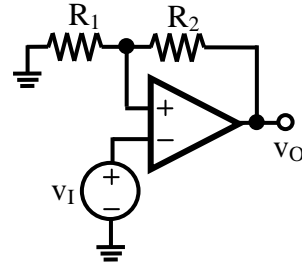


Fig. P5a

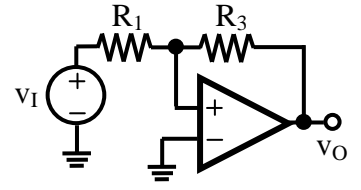


Fig. P5b

(15%) 6. **Fig. P6** shows a NOR-based multivibrator circuit and its waveforms. Assume $R = 100\text{k}\Omega$, $C = 1\text{nF}$, and NOR's transition threshold voltage $V_T = 0.5V_{DD}$.

(a) Which type of multivibrator is it? (bistable/ astable/ monostable) (5%)

(b) Calculate the peak voltage of the V_X , which is labelled as V_P . (5%)

(c) Calculate T_1 . (Hint: RC circuit complete response: $v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$) (5%)

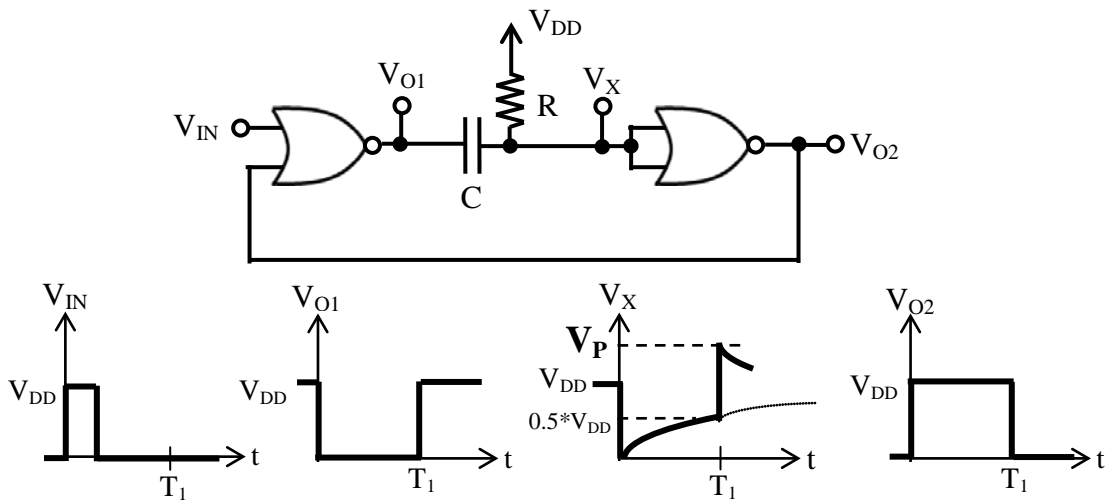


Fig. P6