

# Solution of Mid-term Exam I

Electronics (III) 2011

Prepared by Shih-Hsiung Chien

## Question 1

Taken by Hank EE102A

- With less than 25 words, please list the name of the **four feedback amplifiers** (e.g. Trans... amplifier) and their **corresponding** topologies (e.g. series-shunt). (16%)
  - ◆ Voltage amplifier  $\leftrightarrow$  series-shunt (4%)
  - ◆ Current amplifier  $\leftrightarrow$  shunt-series (4%)
  - ◆ Trans-conductance amplifier  $\leftrightarrow$  series-series (4%)
  - ◆ Trans-impedance amplifier  $\leftrightarrow$  shunt-shunt (4%)
  - ◆ Trans-resistance amplifier


## Question 2

- Consider a closed-loop circuit shown in Fig. P2. Assume that the input impedance of the basic amplifier is **infinite**, open-loop gain  $\mu = 6000$  V/V,  $r_o = R_L = 100$  k $\Omega$ ,  $R_1 = R_2 = 50$  k $\Omega$ ,  $C_L = 1$  pF, please **respectively** calculate the **dc gain of the loop gain**, and the **dominant pole location of the loop gain** by


(a) breaking the loop

at  **$XX'$** . (10%)

 
(b) breaking the loop **at the output of the basic amplifier  $Y$** . (10%)



## Question 2 (cont.)

 

(a)

 


$$|A\beta| = \mu \cdot \frac{R_L // (R_1 + R_2)}{r_o + R_L // (R_1 + R_2)} \cdot \frac{R_1}{R_1 + R_2}$$

$$= 6000 \times \frac{1}{3} \times \frac{1}{2} = \boxed{1000 \text{ (V/V)}}$$

$$f_{p1} = \frac{1}{2\pi \cdot r_{out} C_L}$$

$$\approx \boxed{4.77 \text{ MHz}}$$

(b)

 


$$|A\beta| = \frac{R_1}{R_1 + R_2} \cdot \mu \cdot \frac{R_L // (R_1 + R_2)}{r_o + R_L // (R_1 + R_2)} = \boxed{1000 \text{ (V/V)}}$$


$$f_{p1} = \frac{1}{2\pi \cdot r_{out} C_L} \approx \boxed{4.77 \text{ MHz}}$$



# Question 2 (cont.)

 

(a)

 


$$|A\beta| = \mu \cdot \frac{R_L \parallel (R_1 + R_2)}{r_o + R_L \parallel (R_1 + R_2)} \cdot \frac{R_1}{R_1 + R_2}$$

$$= 6000 \times \frac{1}{3} \times \frac{1}{2} = \boxed{1000 \text{ (V/V)}}$$

$$f_{p1} = \frac{1}{2\pi \cdot r_{out} C_L}$$

$$\approx \boxed{4.77 \text{ MHz}}$$

(b)

 

$$|A\beta| = \frac{R_1}{R_1 + R_2} \cdot \mu \cdot \frac{R_L \parallel (R_1 + R_2)}{r_o + R_L \parallel (R_1 + R_2)} = \boxed{1000 \text{ (V/V)}}$$

$$f_{p1} = \frac{1}{2\pi \cdot r_{out} C_L} \approx \boxed{4.77 \text{ MHz}}$$

### Question 3

- Please give definitions of the following terms for an op amp.

(a) -3dB bandwidth (5%)

the frequency at which the gain is attenuated by 3dB, it is also located at the dominant pole frequency.

(b) unity-gain bandwidth (5%)

the frequency at which the gain drops to unity.

(c) CMRR (5%)

ratio of differential gain to common-mode gain

$$\equiv CMRR = \frac{A_{dm}}{A_{cm}}$$

Question 3 (cont.)

(d) PSRR (5%)

$$\begin{cases} PSRR^+ \equiv \frac{A_d}{A^+} \\ PSRR^- \equiv \frac{A_d}{A^-} \end{cases}, \text{ where } \begin{cases} A^+ \equiv \frac{v_o}{v_{dd}} \\ A^- \equiv \frac{v_o}{v_{gnd}} \end{cases}$$

 $A_d \equiv$  small-signal differential gain $A^+ \equiv$  small-signal gain from the positive **supply** rail to the output $A^- \equiv$  small-signal gain from the negative **supply** rail to the output

## Question 4

Taken by Hank EE102A

- Fig. P4 shows a two-stage op amp with a simple bias circuit. Assume  $\mu_n C_{ox} = 200 \mu A/V^2$ ,  $\mu_p C_{ox} = 80 \mu A/V^2$ ,  $|V_{tp}| = 0.8V$ , and  $I_{D8} = 20 \mu A$ ,  $I_{D5} = 200 \mu A$ ,  $I_{D7} = 500 \mu A$ , and  $(W/L)_{M5} = (20 \mu m / 1 \mu m)$ ,  $(W/L)_{M7} = (50 \mu m / 1 \mu m)$ ,  $(W/L)_{M3} = (10 \mu m / 1 \mu m)$ . Without considering the channel-length modulation, please

(a) calculate  $(W/L)_{M8}$ . (5%)

current mirror between M8 and M5


$$\Rightarrow \left(\frac{W}{L}\right)_{M8} : \left(\frac{W}{L}\right)_{M5} = I_{D8} : I_{D5} \Rightarrow \boxed{\left(\frac{W}{L}\right)_{M8} = \left(\frac{2 \mu m}{1 \mu m}\right)}$$

(b) calculate  $R_b$ . (5%)

$$I_{D8} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_{M8} V_{OV8}^2$$

$$\Rightarrow V_{OV8} = 0.5V$$

$$\Rightarrow R_b = \frac{3.3 - V_{OV8} - |V_{tp}|}{I_{D8}} = \boxed{100 k\Omega}$$

 



## Question 4 Taken by Hank EE102A

- Fig. P4 shows a two-stage op amp with a simple bias circuit. Assume  $\mu_n C_{ox} = 200 \mu A/V^2$ ,  $\mu_p C_{ox} = 80 \mu A/V^2$ ,  $|V_{tp}| = 0.8V$ , and  $I_{D8} = 20 \mu A$ ,  $I_{D5} = 200 \mu A$ ,  $I_{D7} = 500 \mu A$ , and  $(W/L)_{M5} = (20 \mu m/1 \mu m)$ ,  $(W/L)_{M7} = (50 \mu m/1 \mu m)$ ,  $(W/L)_{M3} = (10 \mu m/1 \mu m)$ . Without considering the channel-length modulation, please

(a) calculate  $(W/L)_{M8}$ . (5%)

current mirror between M8 and M5


$$\Rightarrow \left(\frac{W}{L}\right)_{M8} : \left(\frac{W}{L}\right)_{M5} = I_{D8} : I_{D5} \Rightarrow \left(\frac{W}{L}\right)_{M8} = \left(\frac{2 \mu m}{1 \mu m}\right)$$

(b) calculate  $R_b$ . (5%)

$$I_{D8} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_{M8} V_{OV8}^2$$

$$\Rightarrow V_{OV8} = 0.5V$$

$$\Rightarrow R_b = \frac{3.3 - V_{OV8} - |V_{tp}|}{I_{D8}} = 100 k\Omega$$

 


# Question 4 (cont.)

(c) design the  $(W/L)_{M6}$  to minimize the input systematic offset if the input stage is perfectly balanced. (5%)

$$I_{D3} : I_{D6} = \left( \frac{W}{L} \right)_{M3} : \left( \frac{W}{L} \right)_{M6}$$

$$I_{D5} : I_{D7} = \left( \frac{W}{L} \right)_{M5} : \left( \frac{W}{L} \right)_{M7} = (2 \cdot I_{D3}) : I_{D6}$$
 
$$\left( \frac{W}{L} \right)_{M6} = \frac{2 \cdot \left( \frac{W}{L} \right)_{M3} \cdot \left( \frac{W}{L} \right)_{M7}}{\left( \frac{W}{L} \right)_{M5}} = \boxed{\frac{50 \mu m}{1 \mu m}}$$



(d) find the output swing of the op amp. (5%)

$$I_{D6} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_{M6} V_{OV6}^2 \Rightarrow V_{OV6} \approx 0.316V$$

output swing :

$$\boxed{0.316V} = V_{OV6} \leq v_{OUT} \leq V_{DD} - V_{OV7} = VDD - V_{OV7} = \boxed{2.8V}$$

## Question 5

- A folded-cascode op amp is shown in Fig. P5 where  $I_{M11}=200\mu A$ ,  $I_{M10}=300\mu A$ , and  $|V_{OV}|$  for all transistors is  $0.2V$ . Assuming  $\lambda_n=0.1V^{-1}$ ,  $\lambda_p=0.2V^{-1}$ ,  $V_{DD}=3.3V$ ,  $V_{tn}=0.8V$ ,  $|V_{tp}|=0.8V$ , and  $C_L=1pF$ , please

(a) calculate **dc gain**. (5%)


$$r_{ds} = \frac{1}{\lambda I_D}, \quad g_m = \frac{2I_D}{V_{OV}}$$

$$A_d = g_{m1} \cdot R_{OUT} = g_{m1} \cdot \left\{ (g_{m4} r_{ds4}) \cdot (r_{ds2} // r_{ds10}) \right\} // [g_{m6} r_{ds6} r_{ds8}] \approx 1m \cdot 625k = \boxed{625(V/V)}$$

(b) calculate **slew rate**. (5%)

$$\text{Slew Rate} = \frac{I_{D11}}{C_L} = \boxed{200 (V / \mu s)}$$

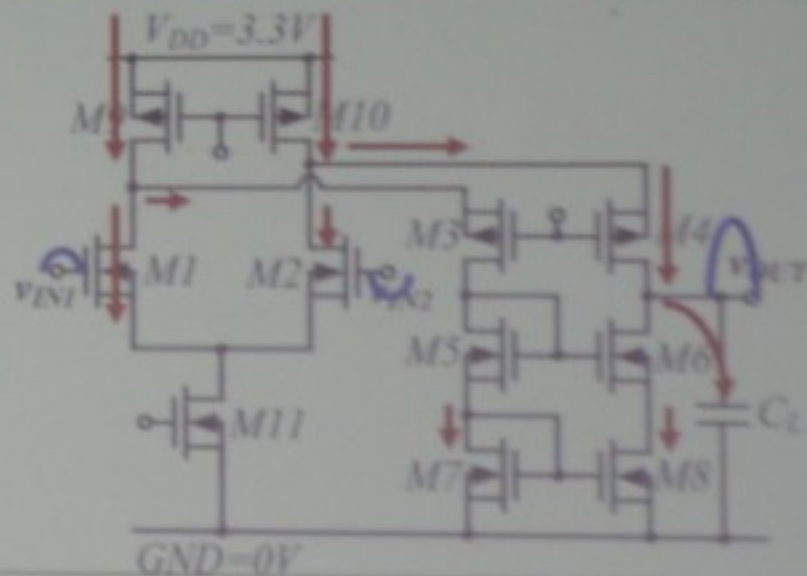(c) specify which node is the **positive** input terminal ( $V_{IN1}$  or  $V_{IN2}$ ).  
Explain your answer. (5%)



- A folded-cascode op amp is shown in Fig. P5 where  $I_{M11}=200\mu A$ ,  $I_{M10}=300\mu A$ , and  $|V_{OV}|$  for all transistors is  $0.2V$ . Assuming  $\lambda_n=0.1V^{-1}$ ,  $\lambda_p=0.2V^{-1}$ ,  $V_{DD}=3.3V$ ,  $V_{tn}=0.8V$ ,  $|V_{tp}|=0.8V$ , and  $C_L=1pF$ , please

(a) calculate **dc gain**. (5%)


$$r_{ds} = \frac{1}{\lambda I_D}, \quad g_m = \frac{2I_D}{V_{OV}}$$

$$A_d = g_{m1} \cdot R_{OUT} = g_{m1} \cdot \left\{ (g_{m4} r_{ds4}) \cdot (r_{ds2} // r_{ds10}) \right\} / [g_{m6} r_{ds6} r_{ds8}] \approx 1m \cdot 625k = \boxed{625V/V}$$

(b) calculate **slew rate**. (5%)

$$\text{Slew Rate} = \frac{I_{D11}}{C_L} = \boxed{200 (V / \mu s)}$$

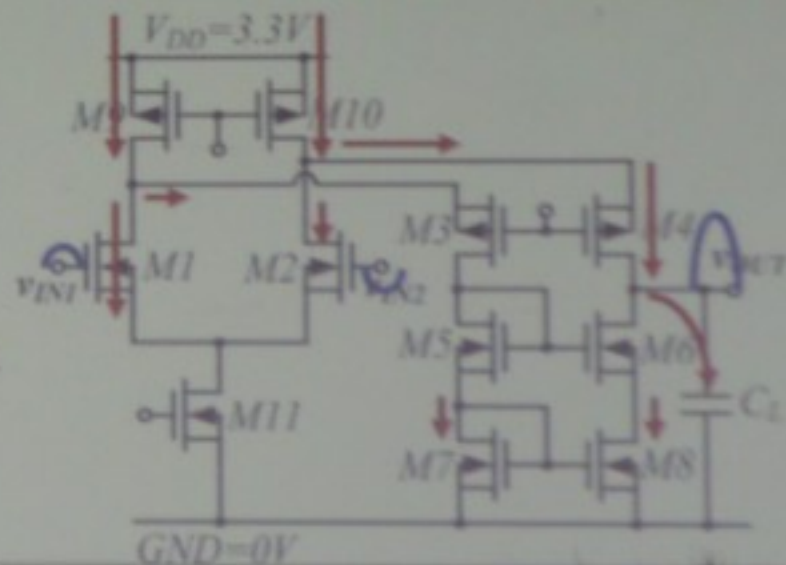(c) specify which node is the **positive** input terminal  $\boxed{v_{IN1}}$  or  $v_{IN2}$ .  
Explain your answer. (5%)



# Question 6

- A wide-swing current mirror is shown in Fig. P6. Assume  $V_{tn}=0.7V$  for all transistors, and  $I_{bias}=I_{in}=I_{out}$ . The  $V_{OV}$  of  $M_1$ ,  $M_2$ ,  $M_3$ ,  $M_4$  are  $0.3V$ . In order to minimize the allowable output voltage,

(a) find  $V_{OV}$  of  $M_5$ . (3%)

$$\text{let } V_{DS1} = V_{DS4} = V_{OV}$$

$$\Rightarrow V_{bias} = 2 \cdot V_{OV} + V_t = 1.3V$$


$$\Rightarrow V_{OV5} = V_{bias} - V_t = 2V_{OV} = \boxed{0.6V}$$

(b) if  $(W/L)_{M1}=(W/L)_{M2}=n_1 \cdot (W/L)_{M3}=n_1 \cdot (W/L)_{M4}=n_2 \cdot (W/L)_{M5}$ , what are the values of  $n_1$  and  $n_2$  should be designed? (6%)

$$I \propto \left( \frac{W}{L} \right) \cdot V_{OV}^2$$

$$\therefore I_{bias} = I_{in} = I_{out} \wedge V_{OV5} = 2 \cdot V_{OV1-4}$$
 
$$\Rightarrow \boxed{\begin{cases} n_1 = 1 \\ n_2 = 4 \end{cases}}$$





## Question 6

Taken by Hank EE102A

- A wide-swing current mirror is shown in Fig. P6. Assume  $V_{tn}=0.7V$  for all transistors, and  $I_{bias}=I_{in}=I_{out}$ . The  $V_{OV}$  of  $M_1, M_2, M_3, M_4$  are  $0.3V$ . In order to minimize the allowable output voltage,

(a) find  $V_{OV}$  of  $M_5$ . (3%)

$$\text{let } V_{DS2} = V_{DS4} = V_{OV}$$

$$\Rightarrow V_{bias} = 2 \cdot V_{OV} + V_t = 1.3V$$

$$\Rightarrow V_{OV5} = V_{bias} - V_t = 2V_{OV} = \boxed{0.6V}$$

(b) if  $(W/L)_{M1}=(W/L)_{M2}=n_1 \cdot (W/L)_{M3}=n_1 \cdot (W/L)_{M4}=n_2 \cdot (W/L)_{M5}$ , what are the values of  $n_1$  and  $n_2$  should be designed? (6%)

$$I \propto \left( \frac{W}{L} \right) \cdot V_{OV}^2$$

$$\because I_{bias} = I_{in} = I_{out} \wedge V_{OV5} = 2 \cdot V_{OV1-4}$$

$$\Rightarrow \begin{cases} n_1 = 1 \\ n_2 = 4 \end{cases}$$

