

系級班別： \_\_\_\_\_ 學號： \_\_\_\_\_ 姓名： \_\_\_\_\_

(無參考資料，可用計算機) 請在答案卷右上方畫上成績欄，謝謝。

- (30%) 1. (a) Consider the input circuit of the 741 op amp of Fig.1a below, when the emitter current of  $Q_8$  is about 20uA. If  $\beta$  of  $Q_1$  is 200 and that of  $Q_2$  is 250, find the input bias current  $I_B$  and the input offset current  $I_{os}$  of the op amp. (10%)
- (b) Design the Widlar current source of Fig.1b to generate a current  $I_{C10}=10\mu\text{A}$  given that  $I_{REF}=1\text{mA}$ , if at a collector current of 1mA,  $V_{BE}=0.7\text{V}$ , find  $V_{BE11}$ ,  $V_{BE10}$ , and  $R_4$ . (10%)
- (c) For a modified 741 whose second pole is at 5MHz. what dominant-pole frequency is required for 45° phase margin with a close-loop gain of 40dB? Assuming  $C_c$  continues to control the dominant pole. What value of  $C_c$  would be required? Assume  $g_m=2\times 10^{-3}$ ,  $A_0=105\text{dB}$  (10%)

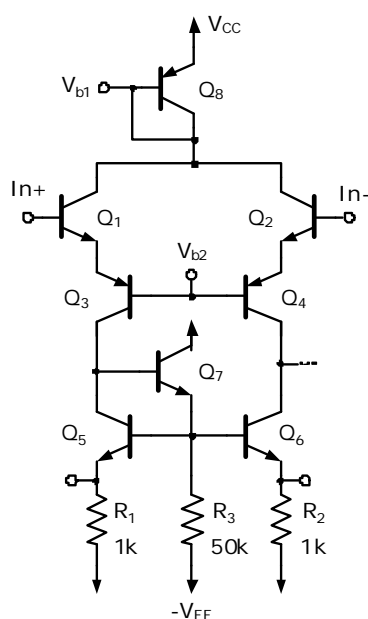


Fig. 1a

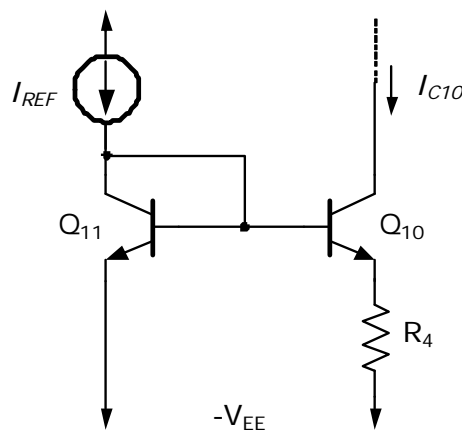


Fig. 1b

- (30%) 2. (a) Find intermediate node voltage at  $V_x$  during the operation of the 3-bit charge-redistribution converter shown in Fig. 2 when  $V_{in}=1.24\text{V}$  and  $V_{ref}=5\text{V}$ . (15%)
- (b) Describe the operational principle of a 2-bit R-2R D/A converter. (15%) (Show figures if necessary)

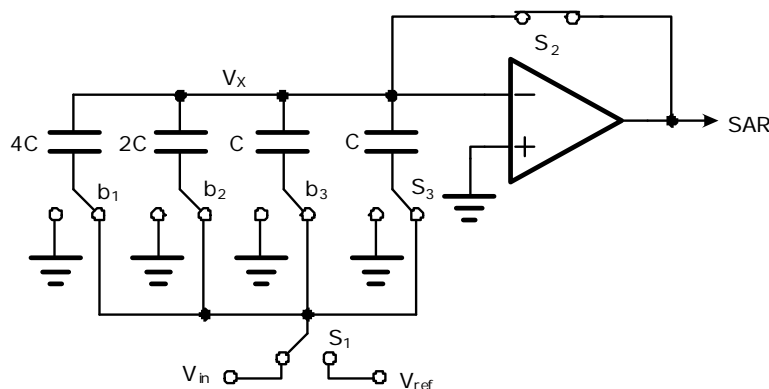


Fig. 2

- (25%) 3. (a) For the emitter follower of Fig. 3, let  $V_{CC}=10V$ ,  $I=100mA$ , and  $R_L=100\Omega$ . If the output voltage is an 8-V-peak sinusoid, find the following: (i) the power delivered to the load (5%) (ii) The average power drawn from the supplies (5%) (iii) The power-conversion efficiency, ignore the loss in  $Q_3$  and  $R$ . (5%)
- (b) Explain why 78.5% maximum efficiency can be achieved by a class-B output stage. (10%) (Show figures if necessary)

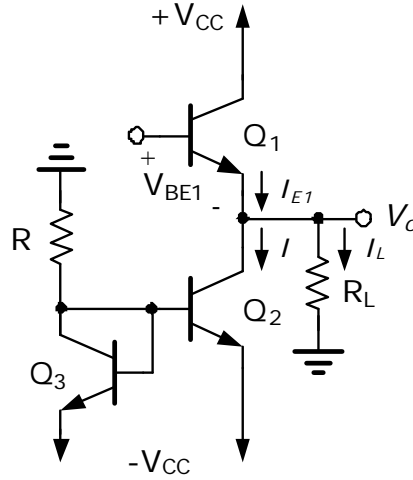


Fig. 3

- (15%) 4. A BJT is specified to have  $T_{Jmax}=150^\circ C$  and to be capable of dissipating maximum power as follows:  
 40W at  $T_C=25^\circ C$ , 2W at  $T_A=25^\circ C$   
 Above  $25^\circ C$ , the maximum power dissipation is to be derated linearly with  $\theta_{JC}=3.12^\circ C/W$  and  $\theta_{JA}=62.5^\circ C/W$ . Find
- (a) The maximum power that can be dissipated safely by this transistor when operated in free air at  $T_A=50^\circ C$ . (5%)
- (b) The maximum power that can be dissipated safely by this transistor when operated at an ambient temperature of  $50^\circ C$ , but with a heat sink for which  $\theta_{CS}=0.5^\circ C/W$  and  $\theta_{SA}=4^\circ C/W$ . Find the temperature of the case and of the heat sink. (5%)
- (c) The maximum power that can be dissipated safely if an *infinite heat sink* is used and  $T_A=50^\circ C$ . (5%)

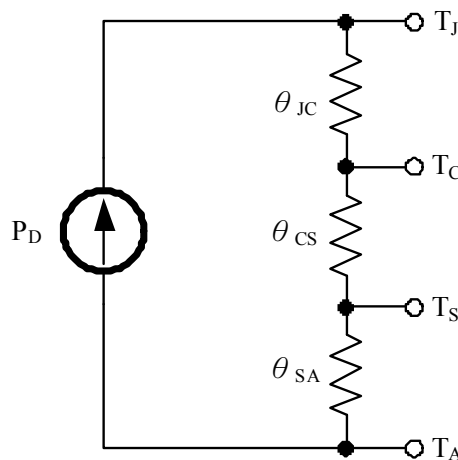


Fig. 4